

# Buttons and Keypads


# Buttons vs keypad

- Button
  - generates logic 0 and 1 values
  - implemented as a switch w/ pull up/down
- Keypad
  - conceptually a matrix of buttons
  - Processed by scanning rows & columns


# Button

- Two conceptual states: on/off
- Implementation:
  - SPDT switch: connects to logic 0 or 1
  - SPST switch: connects to logic 0 or pull
- Issues
  - power consumption, key bounce


# Revisited: EdSim51

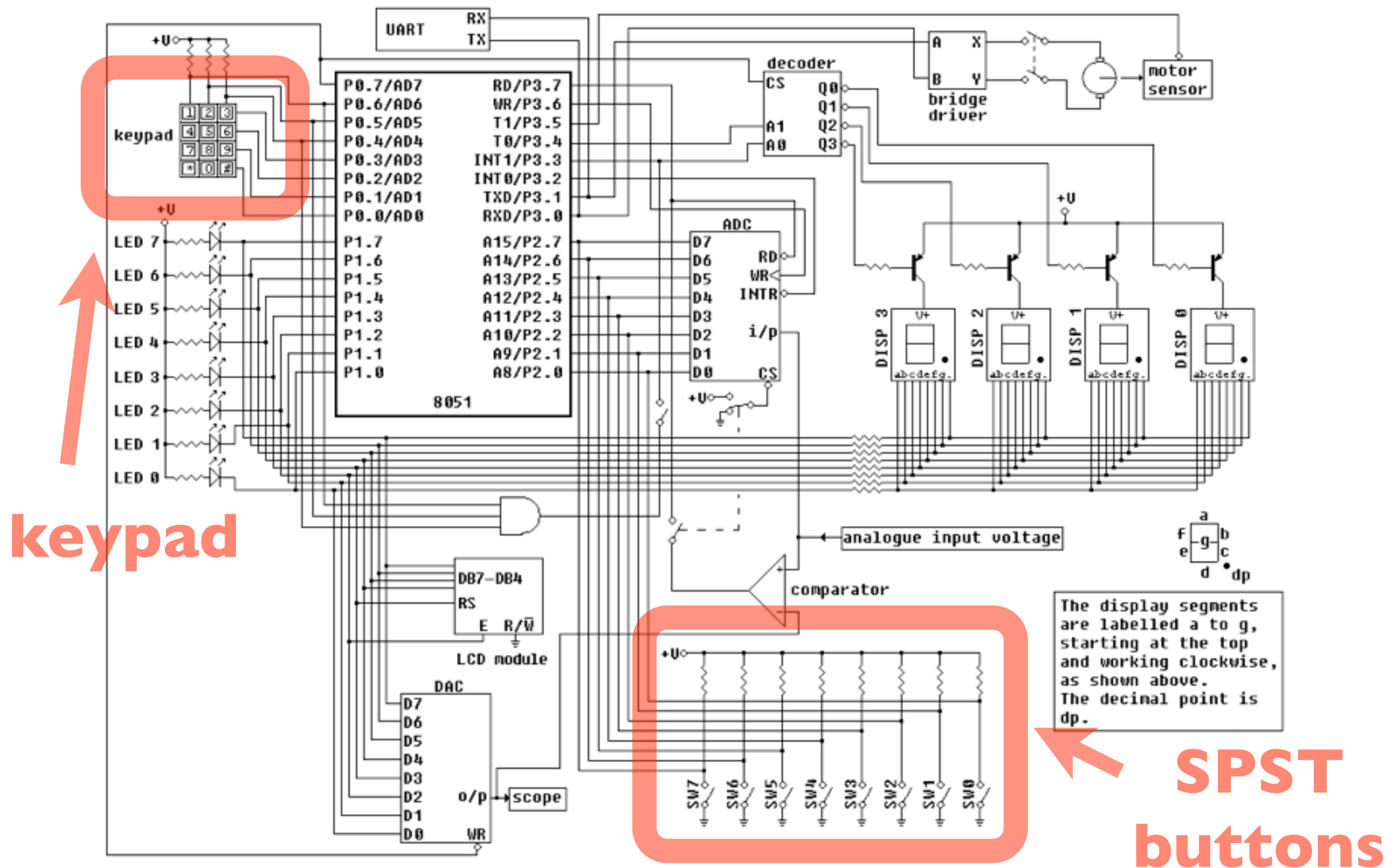

# SPST vs. SPDT

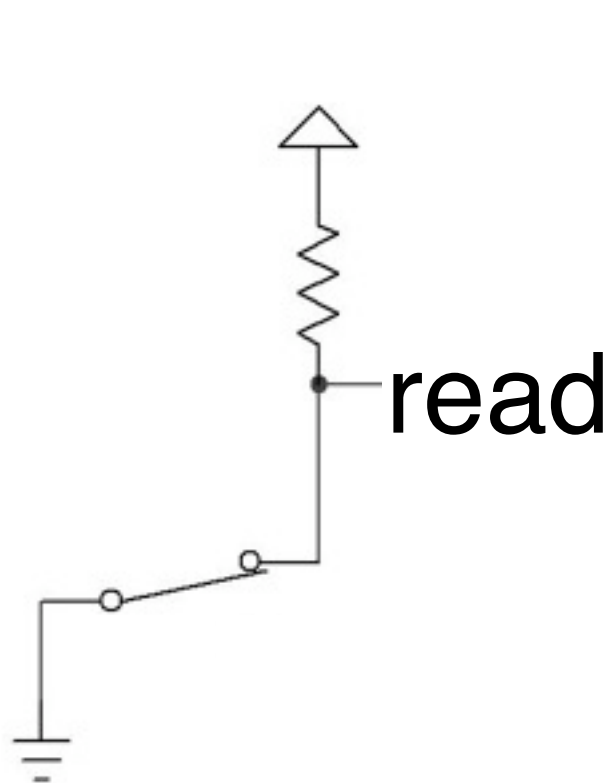

2 states:  
pull up or Gnd

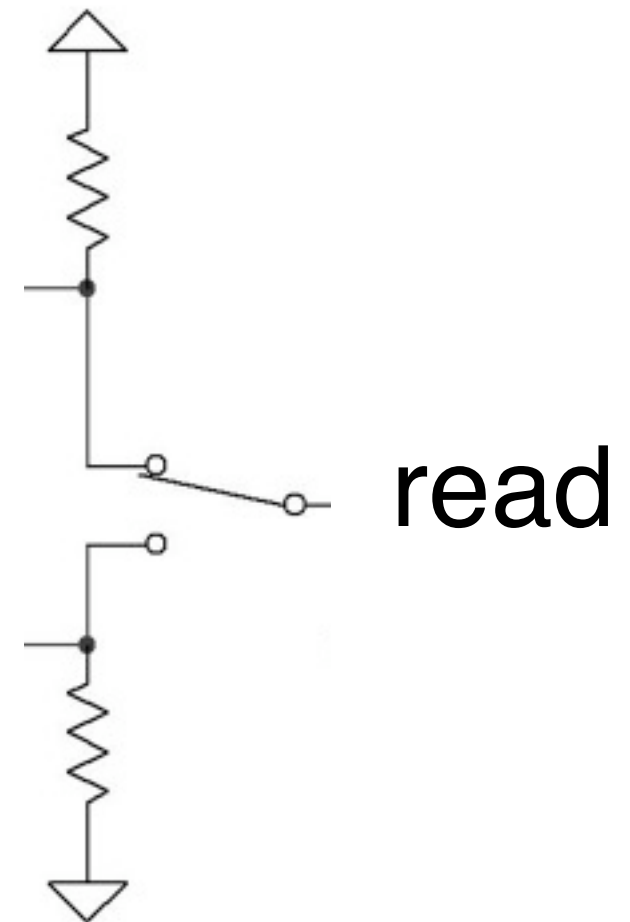


3 states:  
pull up, pull down, and  
in between!

# SPST vs. SPDT

- SPST: simpler
  - consumes virtually no current when open
  - consumes some current when pressed
- SPDT
  - consumes same current when open,
  - consumes **less current** when pressed



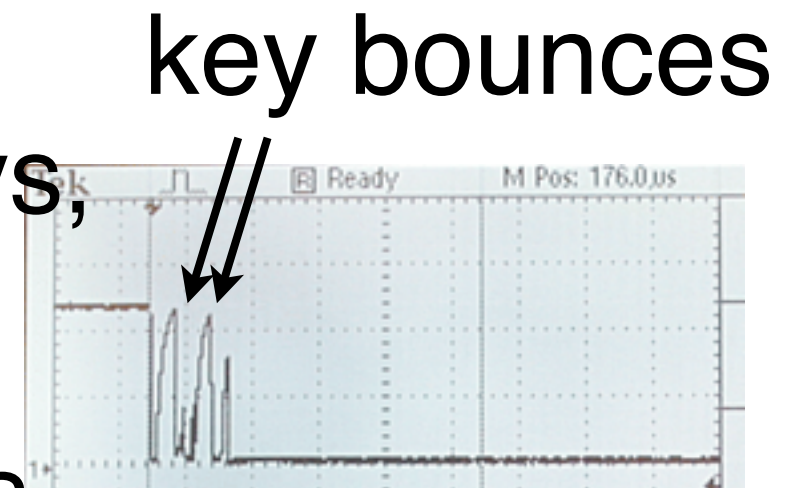
# Key bouncing

- When you press/release keys, could get key bouncing
- User may intend one press, but looks like multiple fast presses
- Solutions:
  - hardware: debouncing switch (cross-coupled NANDs as SR latch)
  - software: **delay** (~20ms)


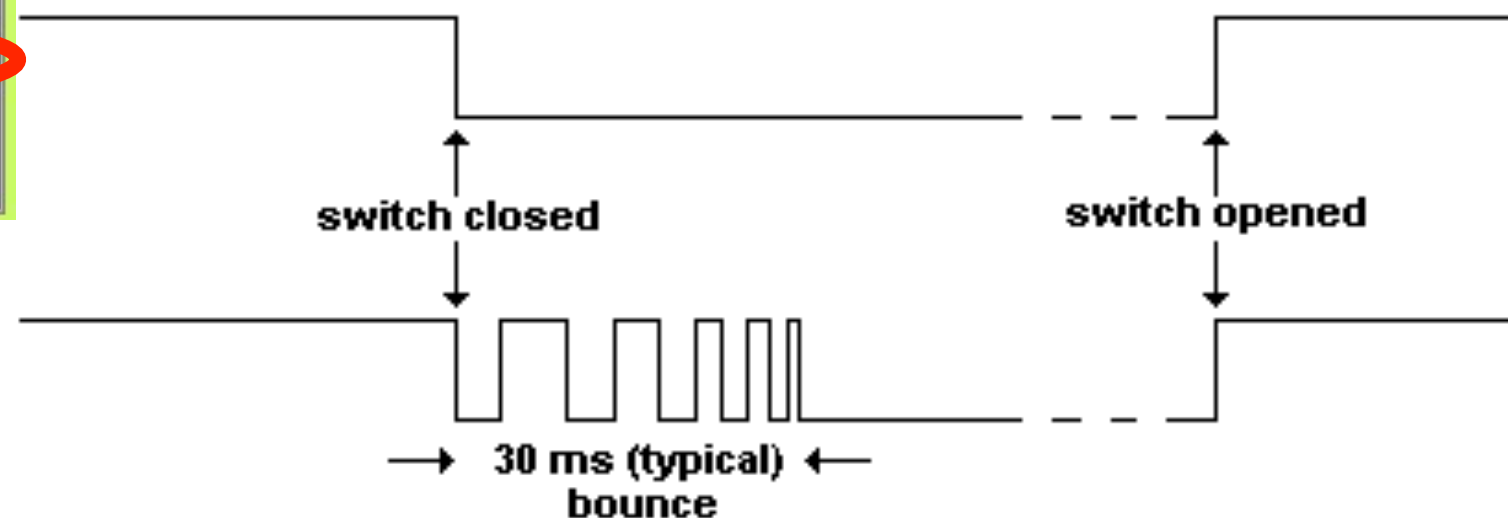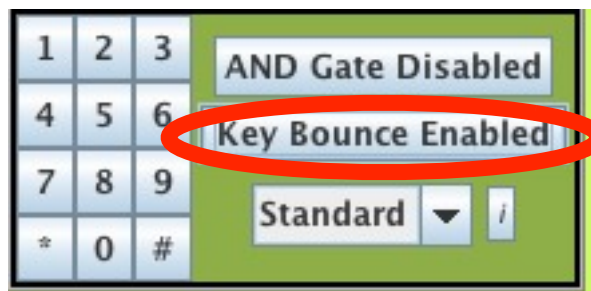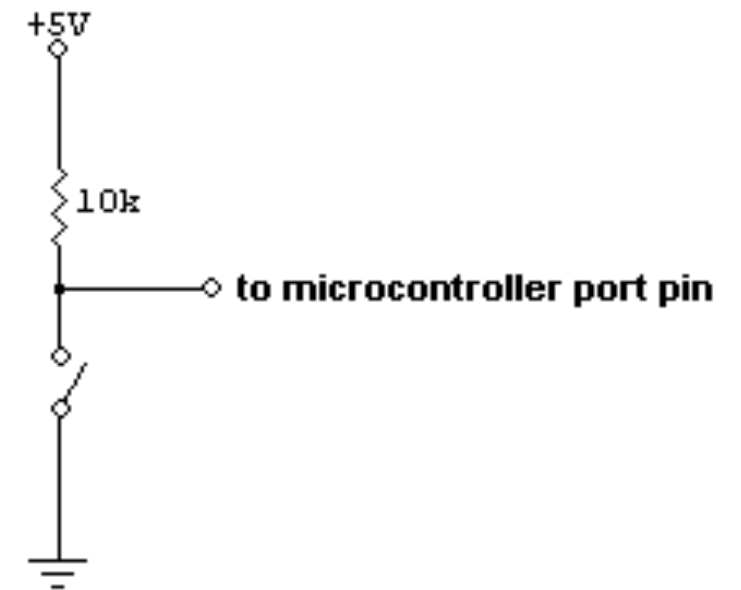
# Key bouncing in EdSim


- Not pressed: pulled high
- Pressed: pulled low
- Can simulate bouncing




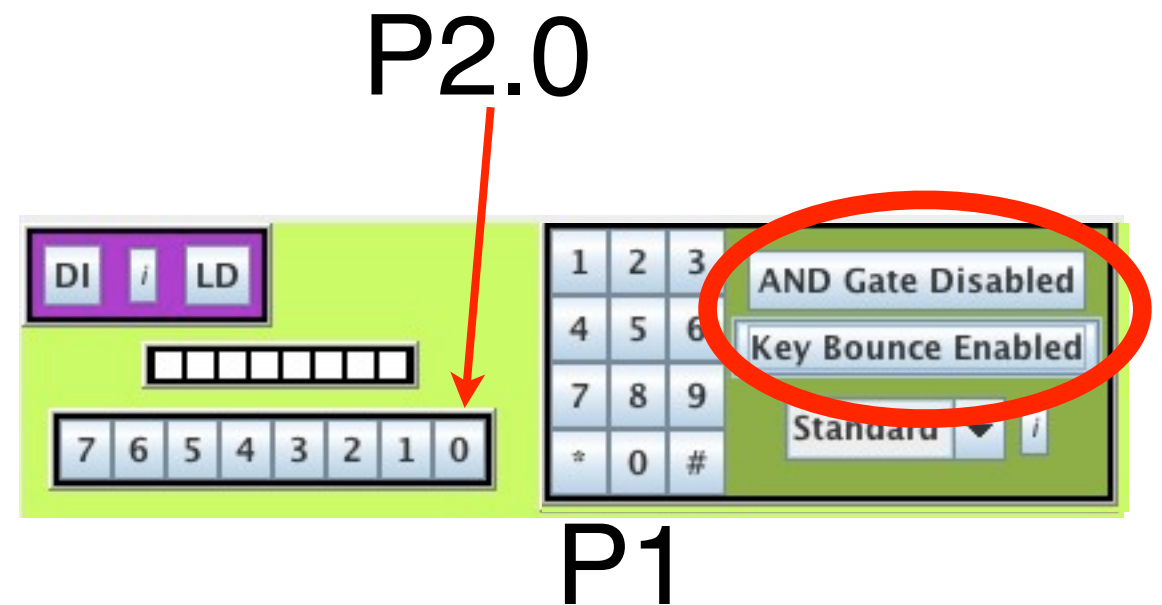
# Key bouncing in EdSim

- Test: use switch#0 (P2.0)
- See how many times it increments on each press/release
- Display using LEDs (P1)





```
notPressed: JB P2.0, notPressed
             ;; increment LED bank, which is P1
             INC P1
             ;; now pressed, wait until button release

pressed:
             JNB P2.0, pressed
             ;; now jump back to beginning
             SJMP notPressed
```


# Hardware Debouncer

- SR Latch with two steady states

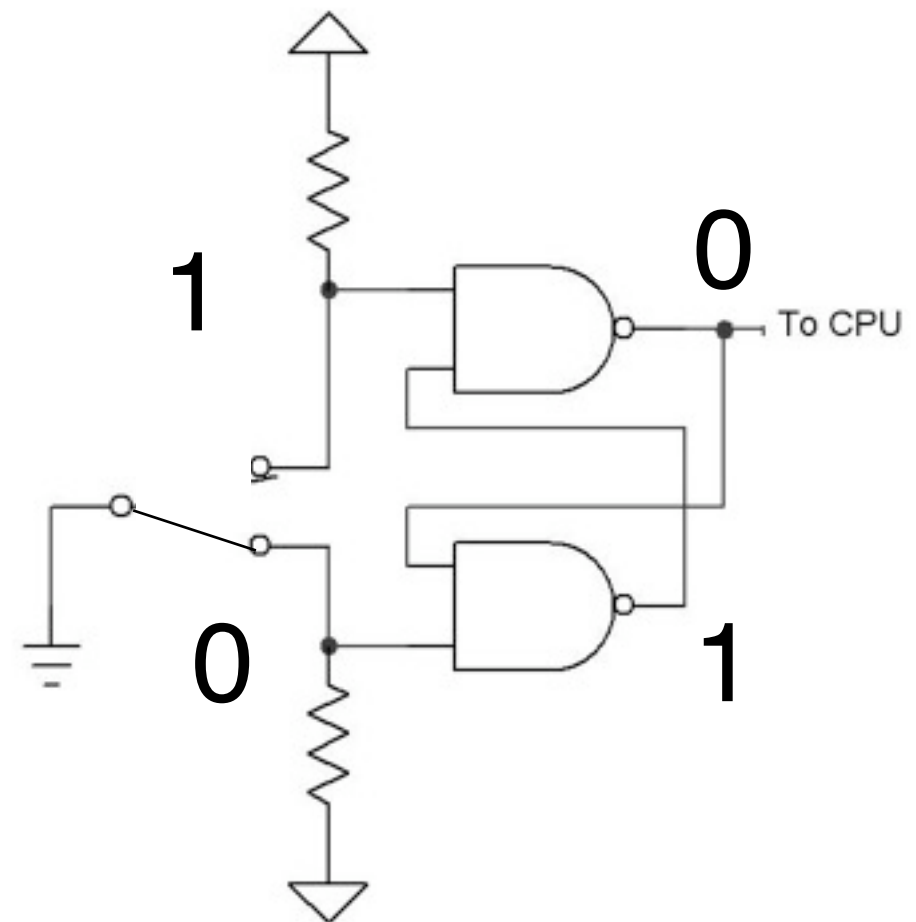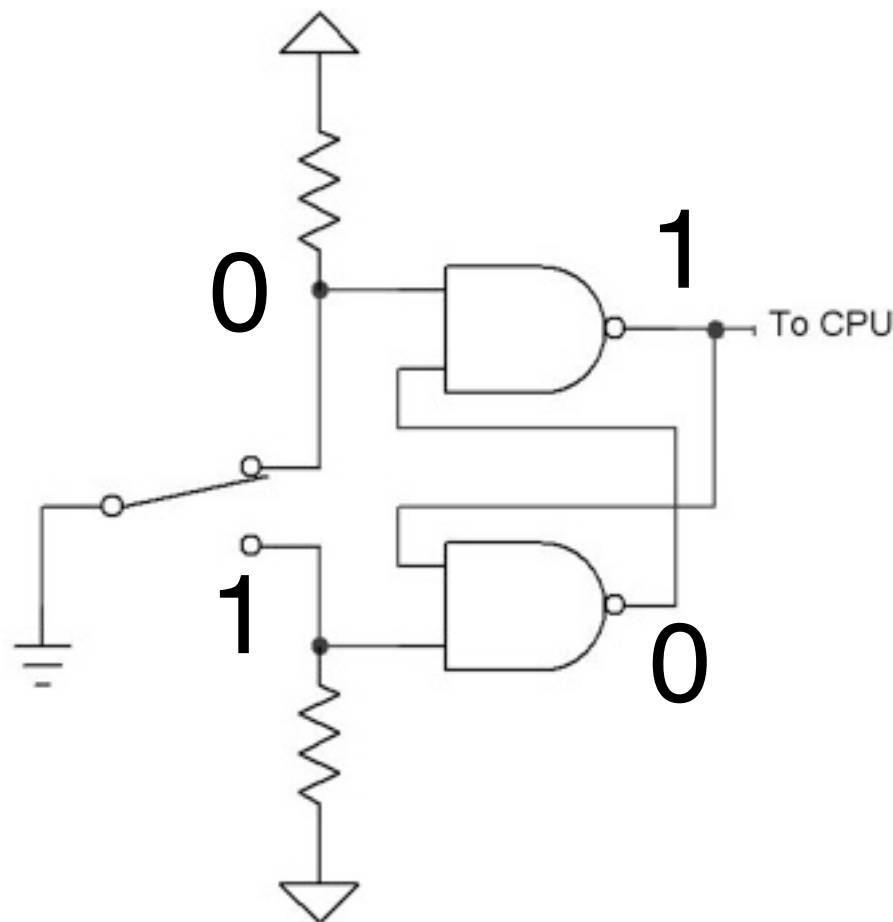

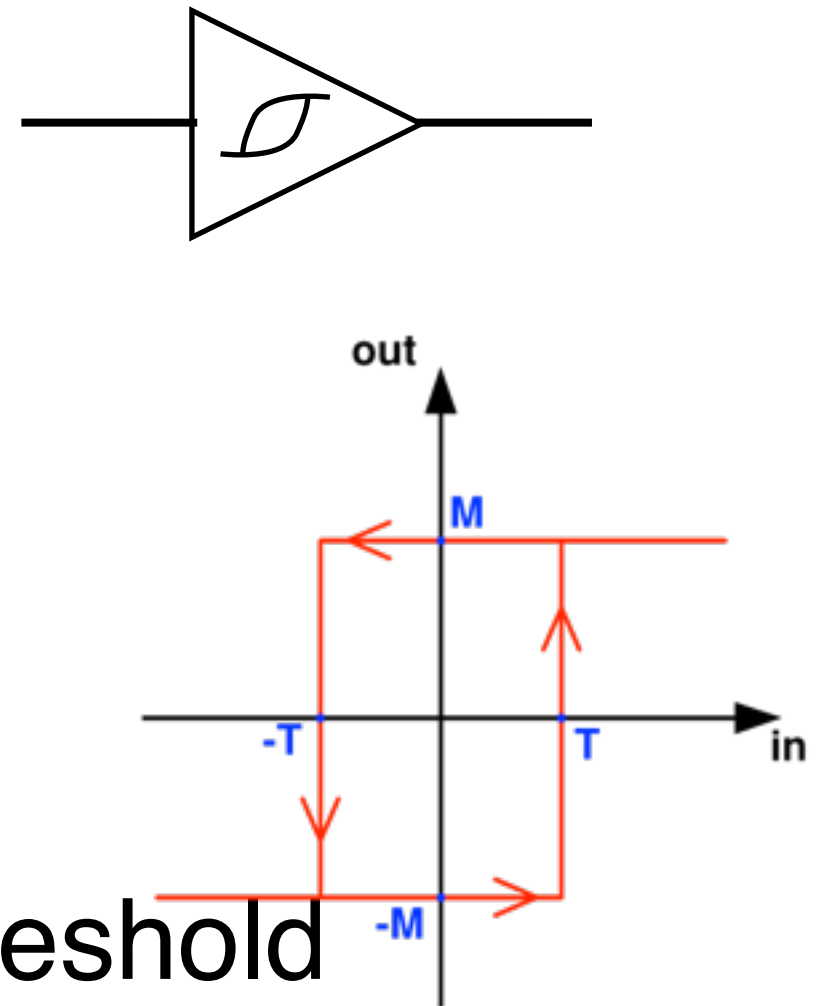
# Debouncing with Schmitt Trigger

- Dual threshold
  - Once it switches state, another threshold applies to switch back to the original state
- Good for debouncing
  - bounce state  $\Rightarrow$  within threshold


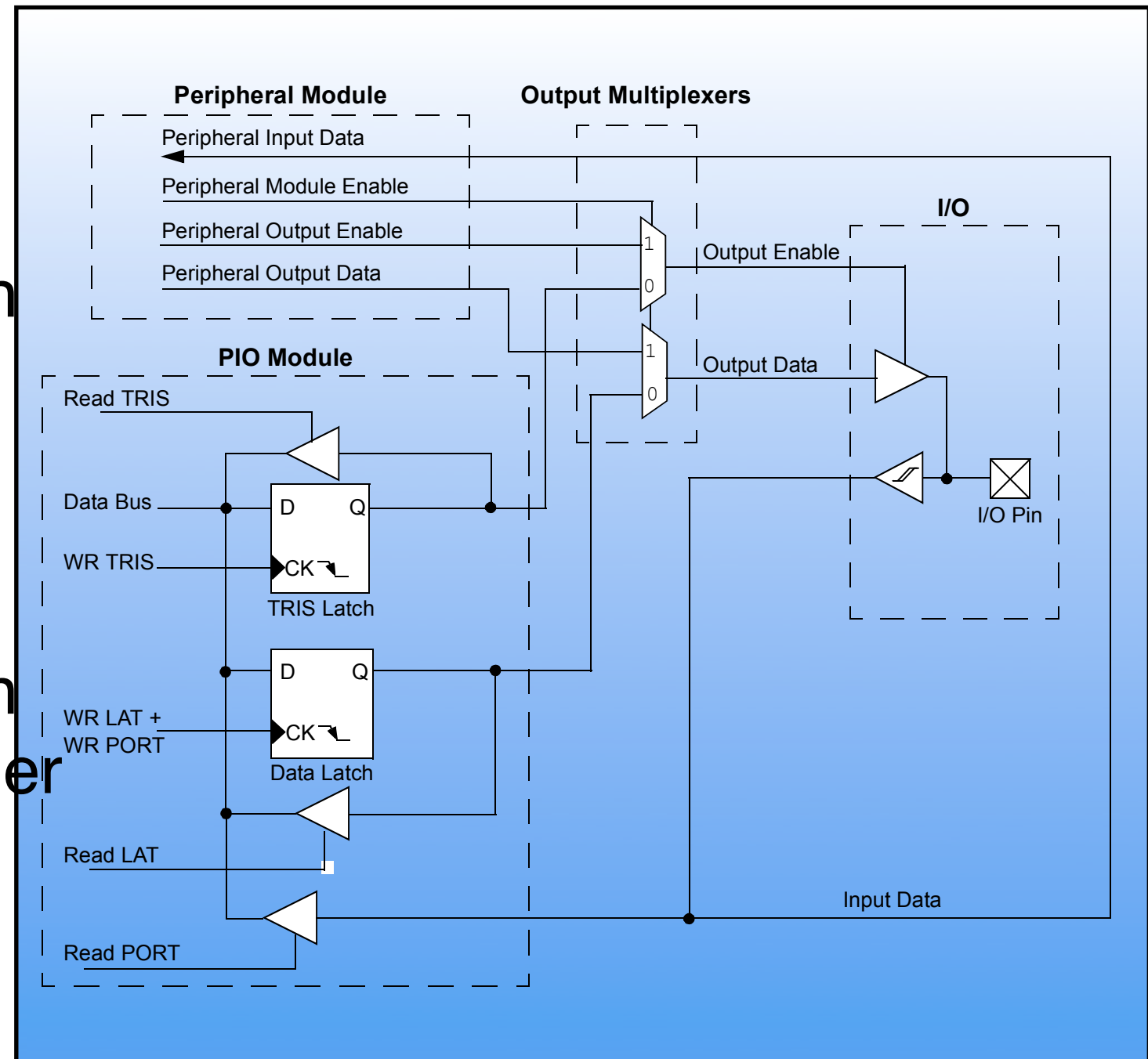
# I/O port schematic for the PIC24

- Output enable
  - puts value of latch onto the pin (pad)
- Input
  - reads from the pin after Schmitt trigger (dual threshold)



# Software Debouncing

- Just delay for 10-30ms before checking the switch again
- Advantage: No need for extra hardware
- Disadvantage: busy loop can be wasteful
- Solution: use timer interrupt (later)


# Keypad interfacing

- Keypad = matrix of push buttons
- Interface Option 1: one bit per key
  - +: enables  $2^n$  combinations of key presses
  - -: needs  $n$  I/O pins  $\Rightarrow$  not scalable!  
(computer keyboards  $\Rightarrow$  101 keys)
- Option 2: row/column scanning
  - Grows by  $\sqrt{n} * 2$



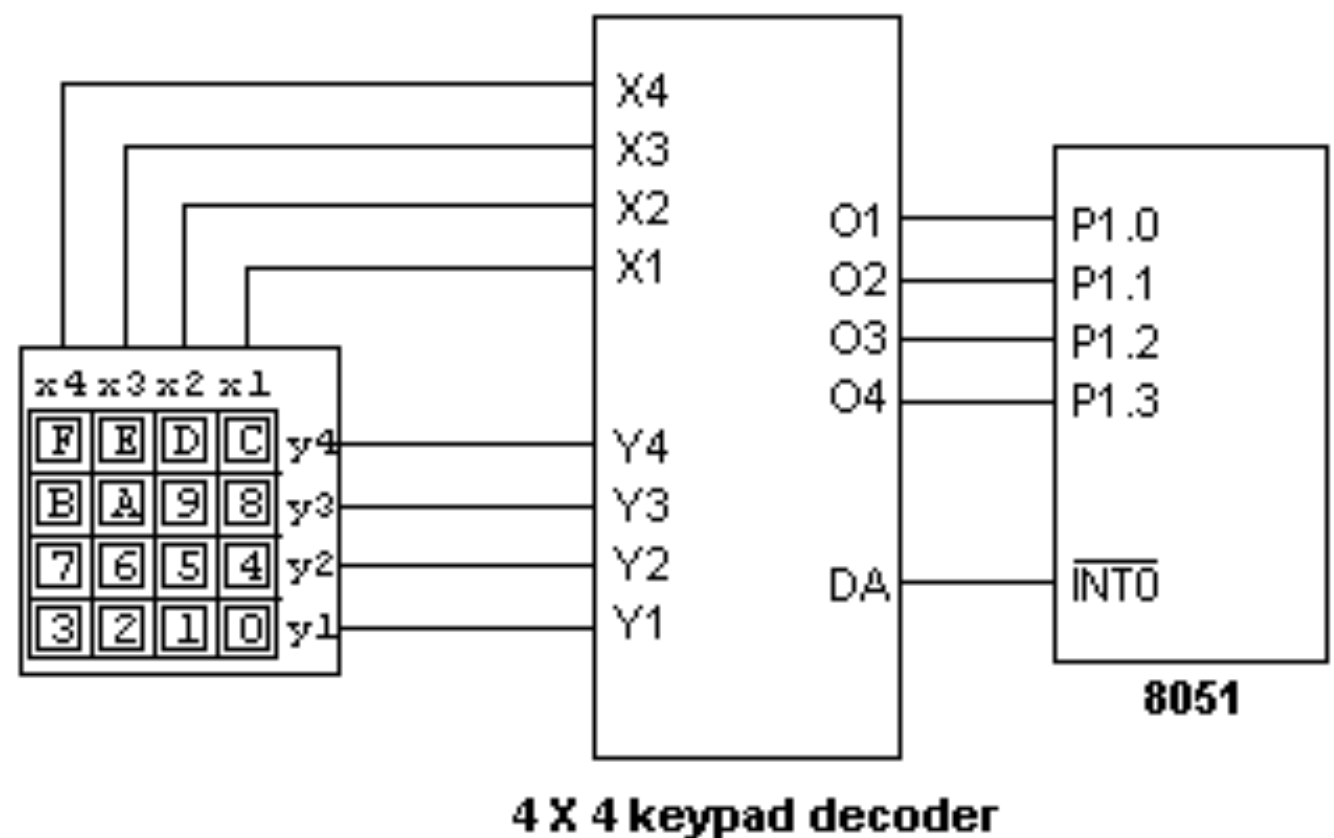
# Hardware "decoder" for Keypad

- Encodes 16 keys using 4 bits to the MCU
- Handles debouncing
- DA (data available)
- Goes low when any key pressed
- Goes high when all released



# Truth table for Decoder


X:Y	O<4:1>
0001 0001	0000
0001 0010	0001
0001 0100	0010
0001 1000	0011
0010 0001	0100
0010 0010	0101
0010 0100	0110
0010 1000	0111
0100 0001	1000
0100 0010	1001
0100 0100	1010
0100 1000	1011
1000 0001	1100
1000 0010	1101
1000 0100	1110
1000 1000	1111

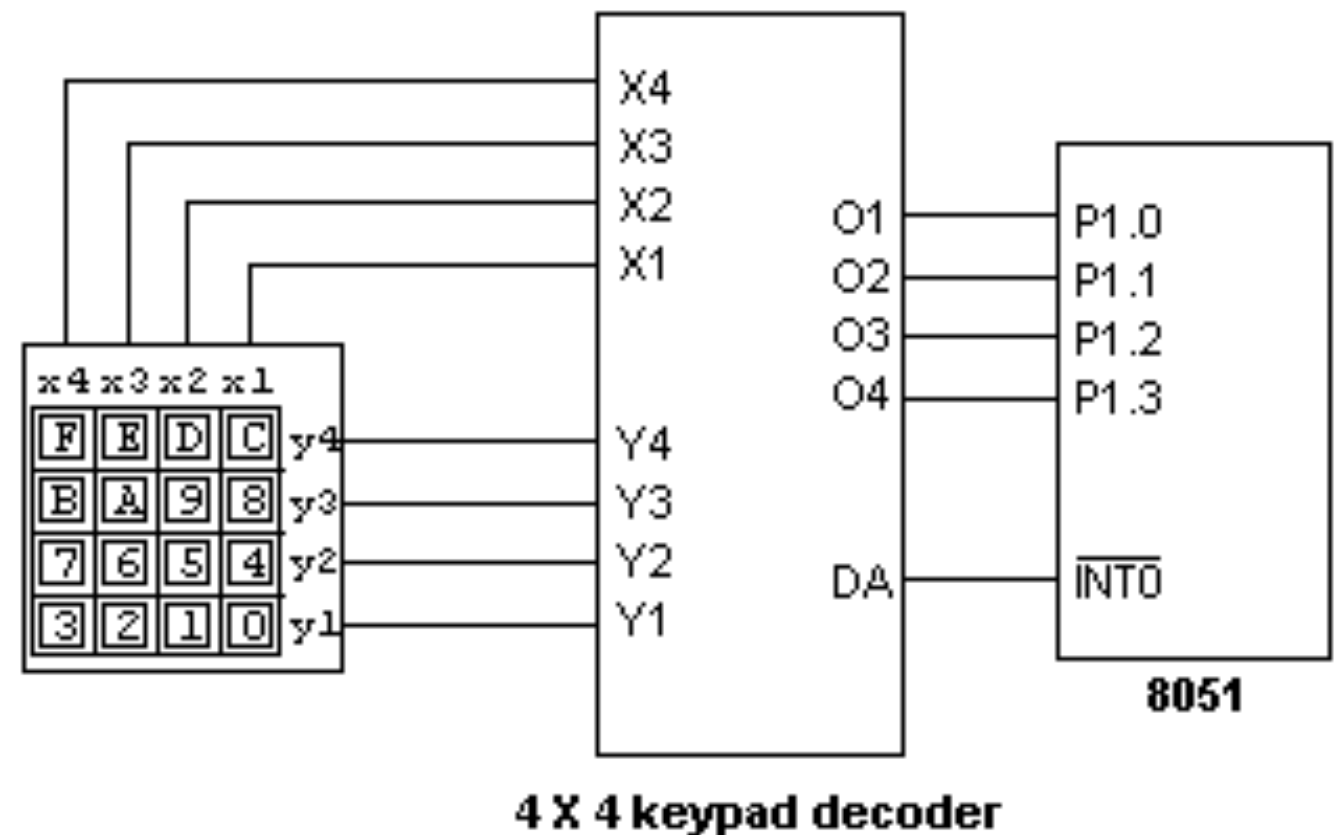



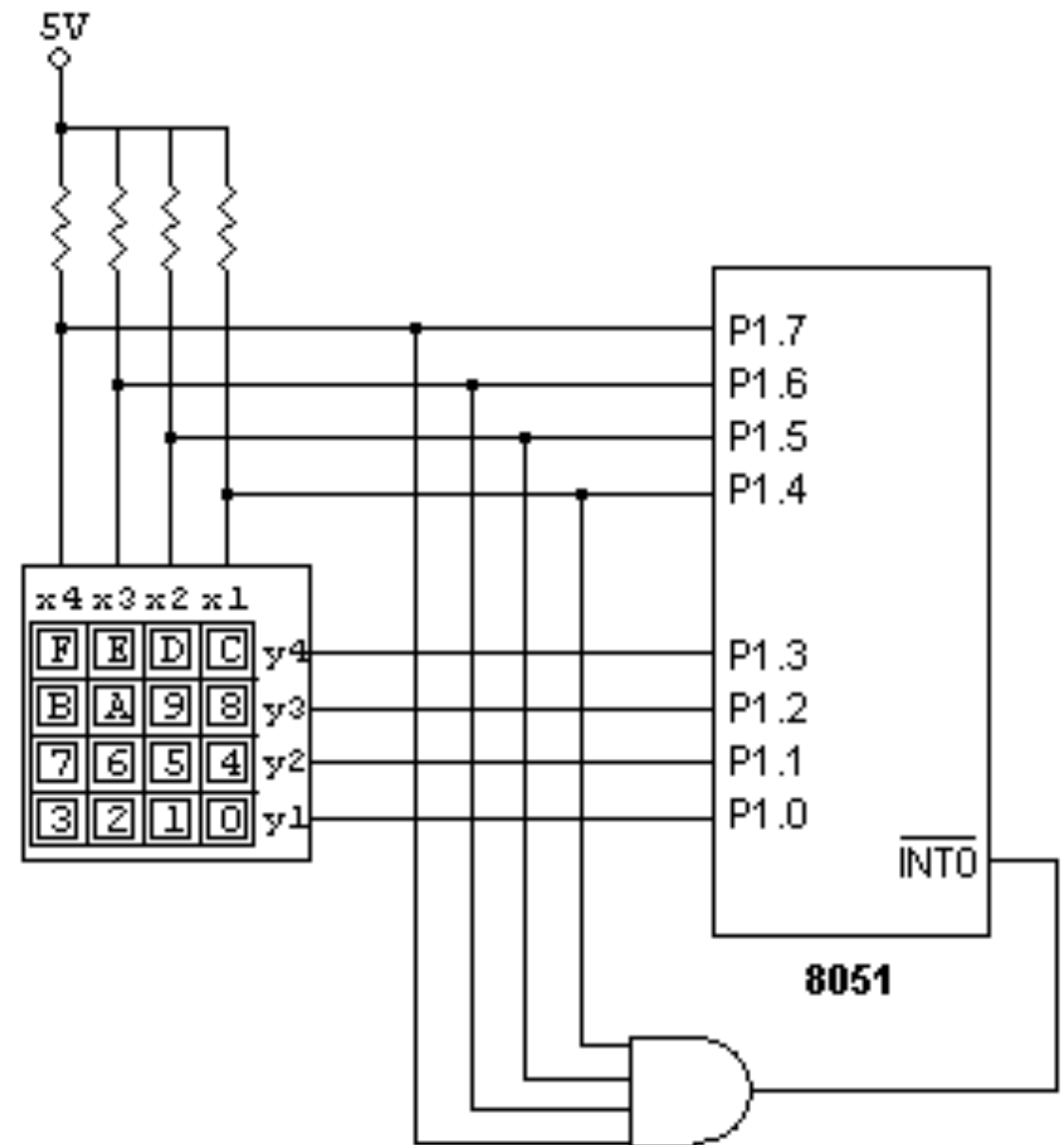
# Software Decoder

- Scan one row at a time by setting that row to 0
- Scan each column if 0, then pressed if 1, then not pressed
- DA line (optional) indicates if ANY key is pressed.



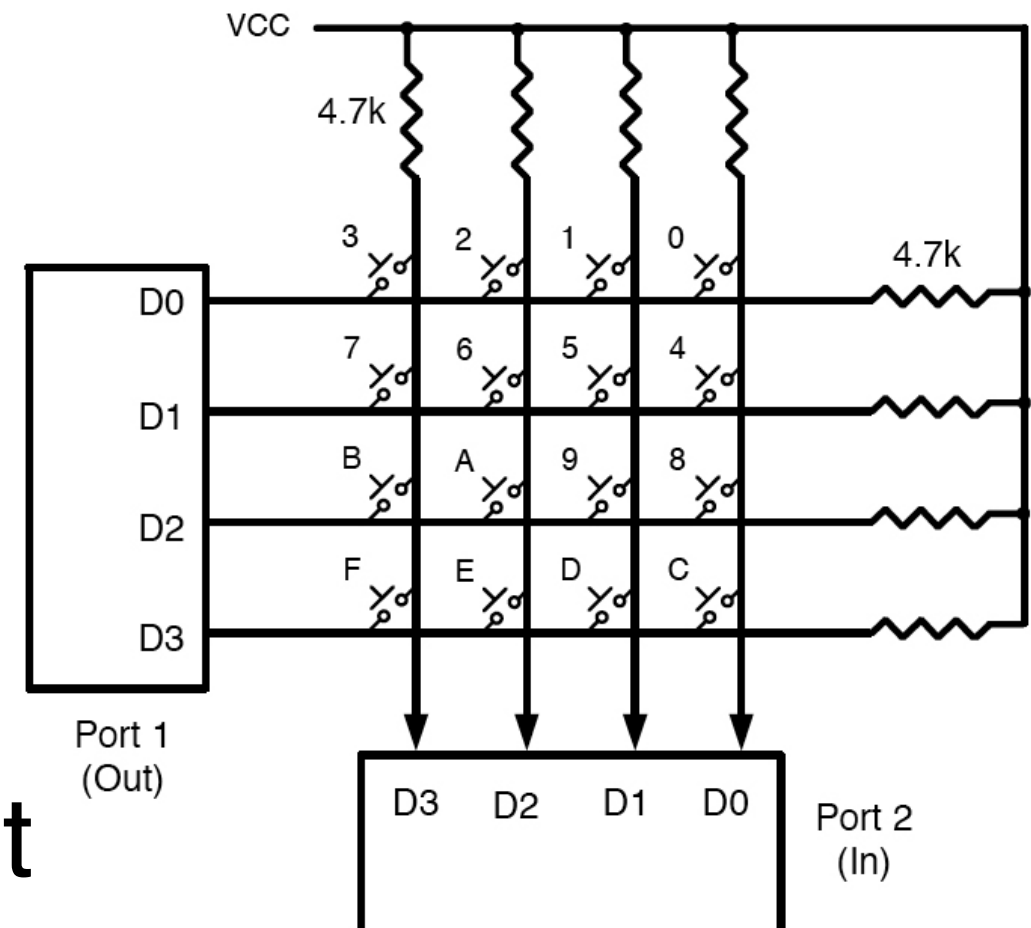
# 4x4 key matrix

- Pull-up lines
- Press => connects Row & Column
- Connection
  - Rows: MCU output
  - Columns: MCU input



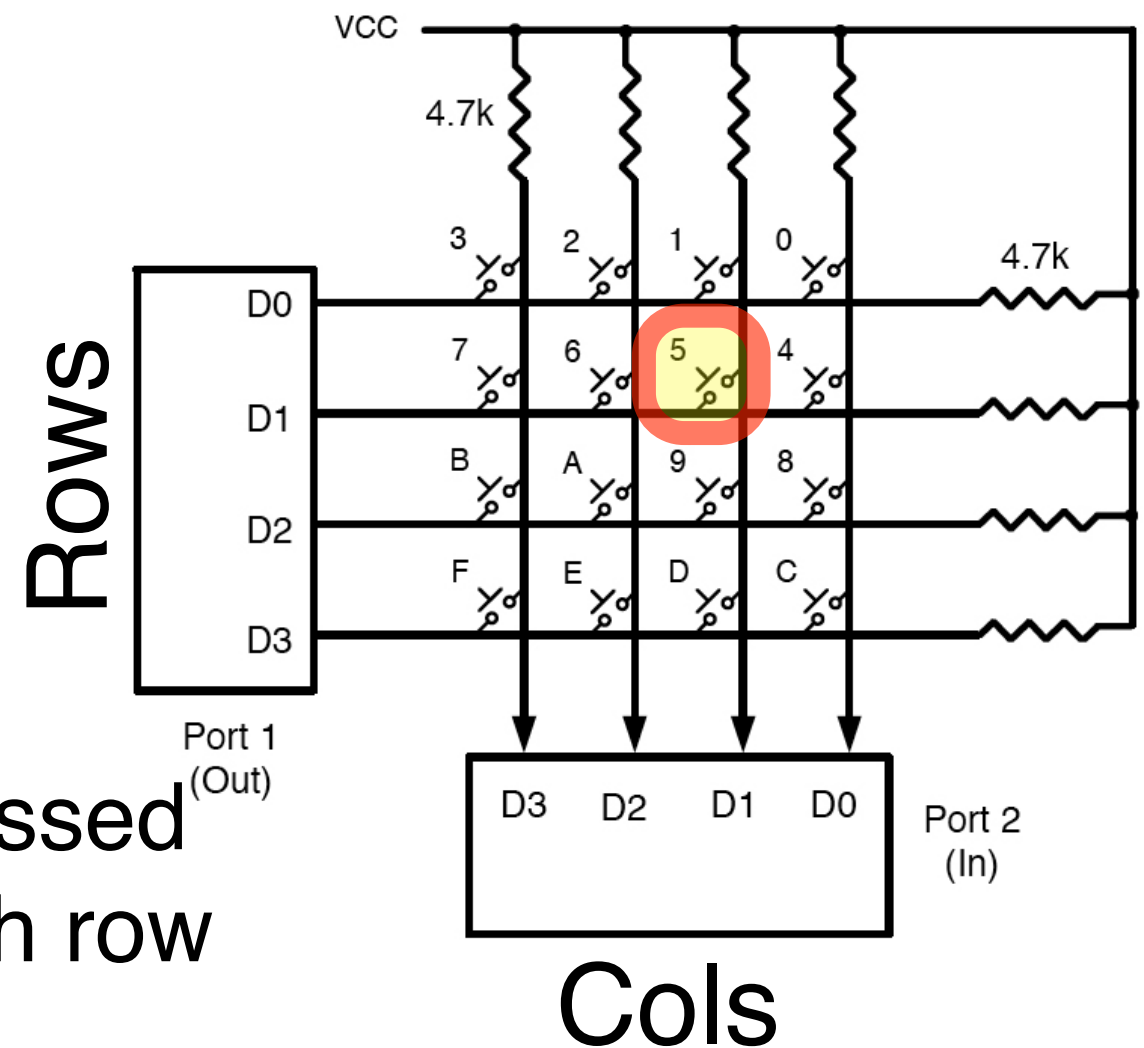
# Key-press detection

- MCU sets  
Rows(output)=0000
- If no press,  
Cols(input)==1111
- If (key 5 is pressed),  
Cols(input) ==1101
- Still need to find  
which Row(s) got pressed  
=> serially check each row


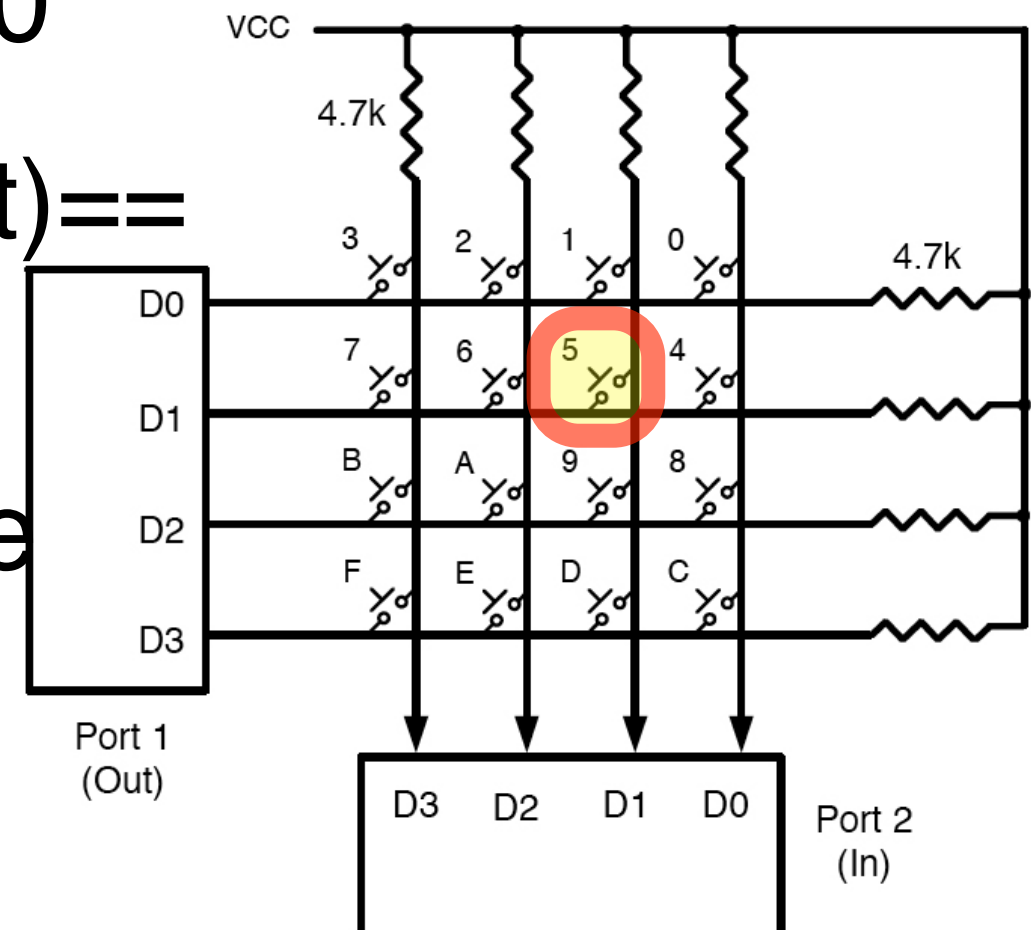
# Serially checking each row (for given col)


- MCU sets Rows(output)= 0111, 1011, 1101, 1110
- MCU reads Cols(input)== 1111, 1101, 1111, 1111
- 0s yield the coordinate of the pressed button => multi-button press can be detected too!



# Software debouncing for Keypad


- you can still do software debouncing
- Option 1: check DA line like a button
- Option 2: while scanning row/col
  - start busy waiting as soon as you find one
  - Issue: compatible with multiple keys?

# Flowchart for keypad scanning

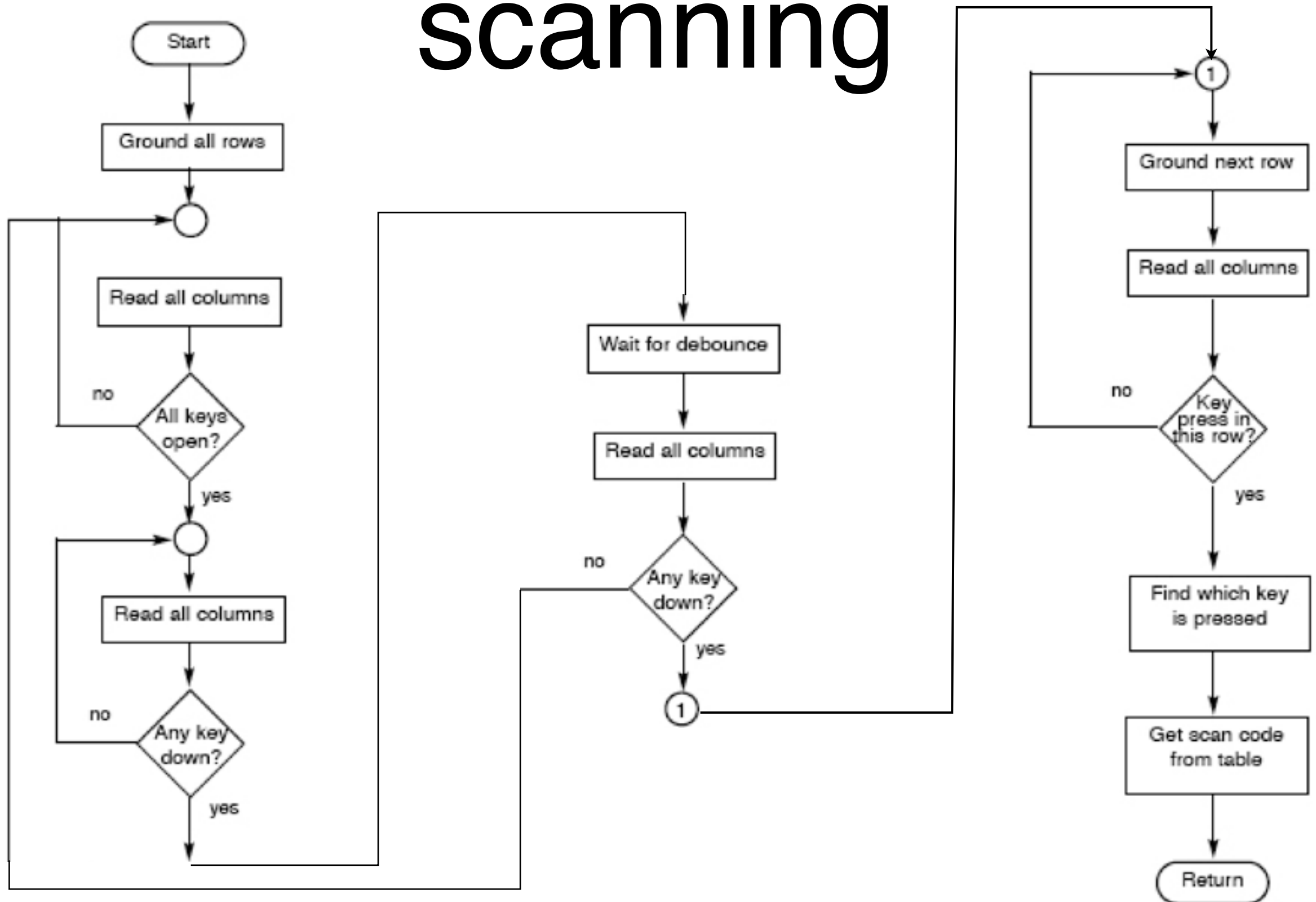
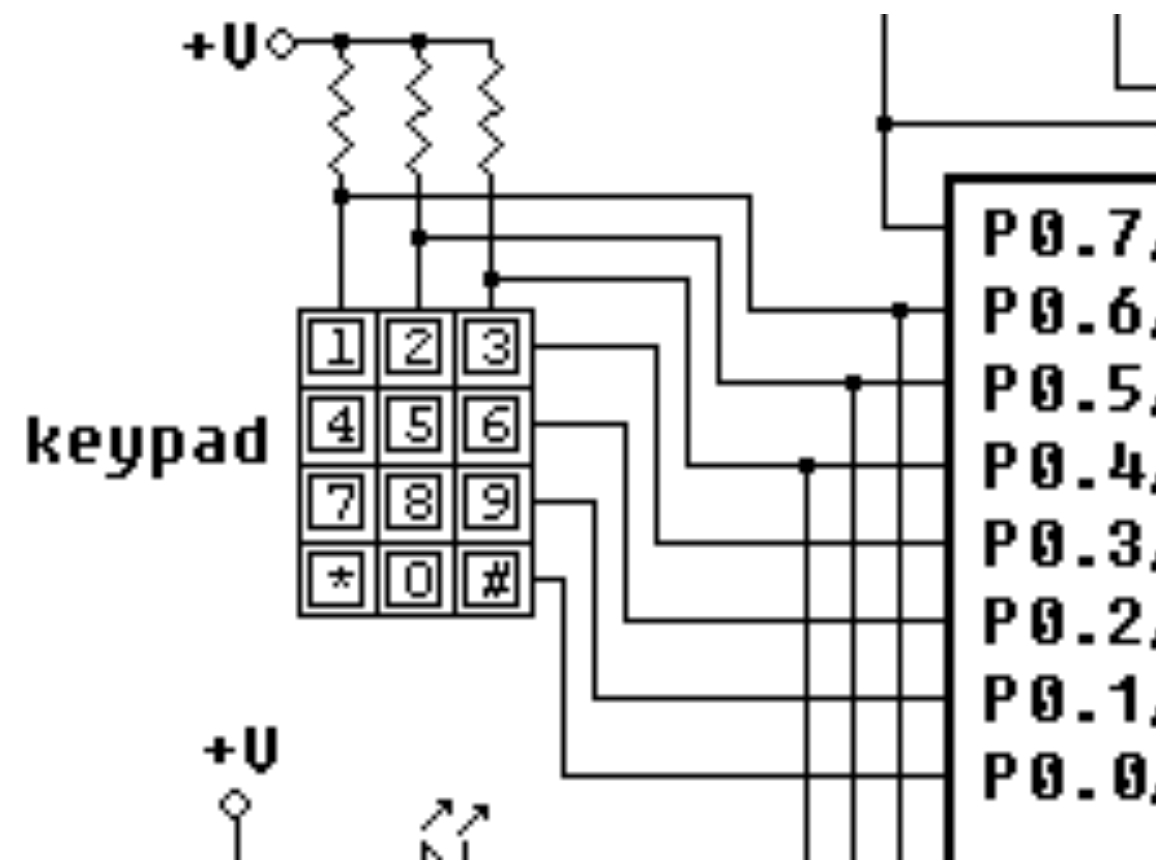
# Keypad in EdSim51

- Set P0.4-P0.6 to 111
  - to enable input of columns
- Take turn setting P0.0-P0.3 to 0 one bit at a time
  - to select a row




# scankey.c

```
#include <8051.h>
char colScan(char c);
void Main(void) {
    char bitmap, bitmapL, bitmapH; char row, rowmask;
    while (1) {
        for (row=bitmapL=bitmapH=0, rowmask = 0xf7; row < 4; row++, rowmask >>= 1) {
            bitmap=colScan(0xFE);
            if (row==2) {
                bitmapH = (bitmapL >> 2);
            }
            bitmapL = (bitmapL<<3) | bitmap;
        }
        P1 = bitmapL;
        P2 = bitmapH;
    }
}


char colScan(char rowmask) {
    P0 = rowmask;
    return (~(P0>>4)) & 0x07;
}
```



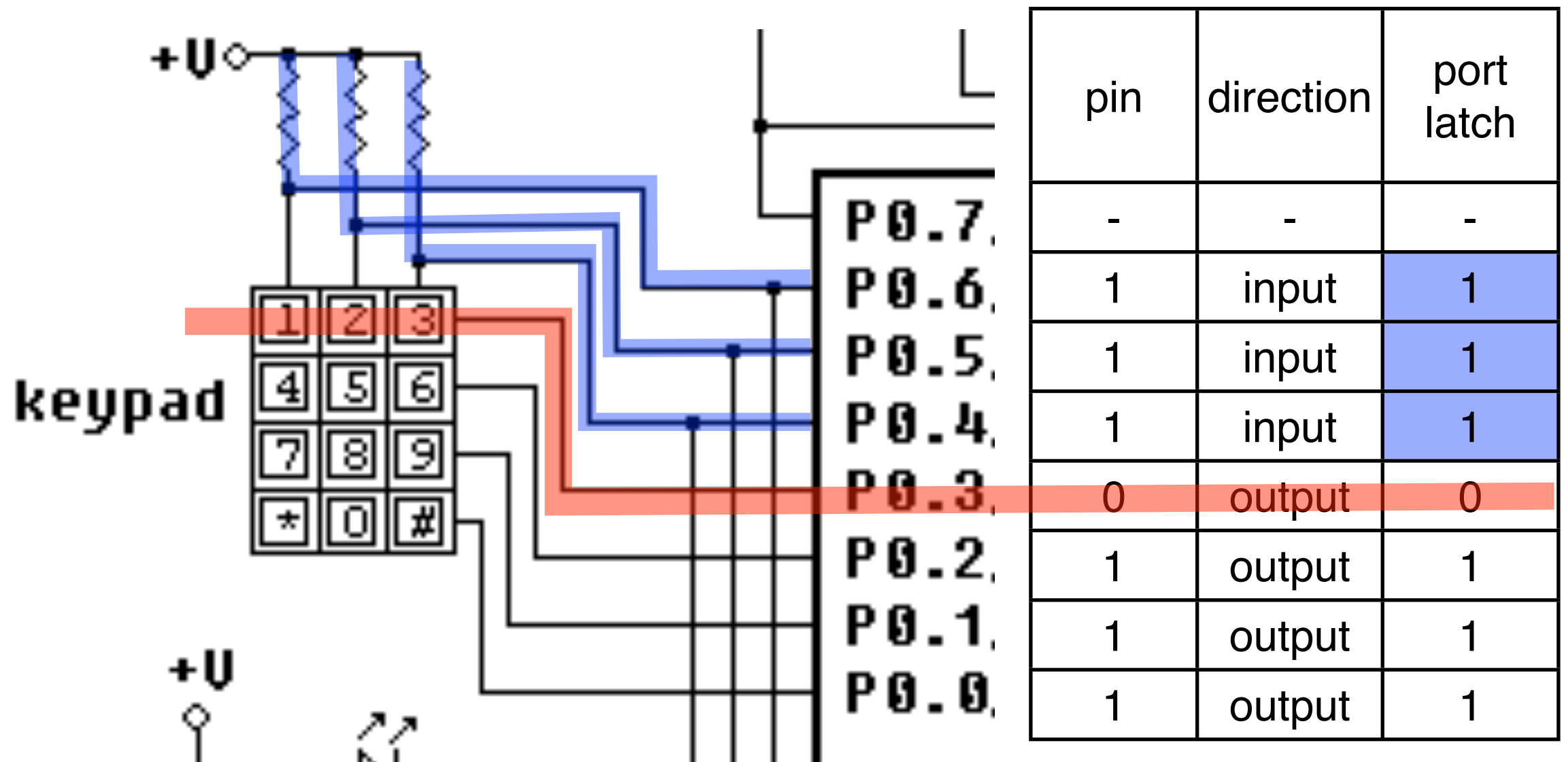
# To test row 0 (keys 1,2,3) when no key pressed




# Testing row 0 while key [1] pressed

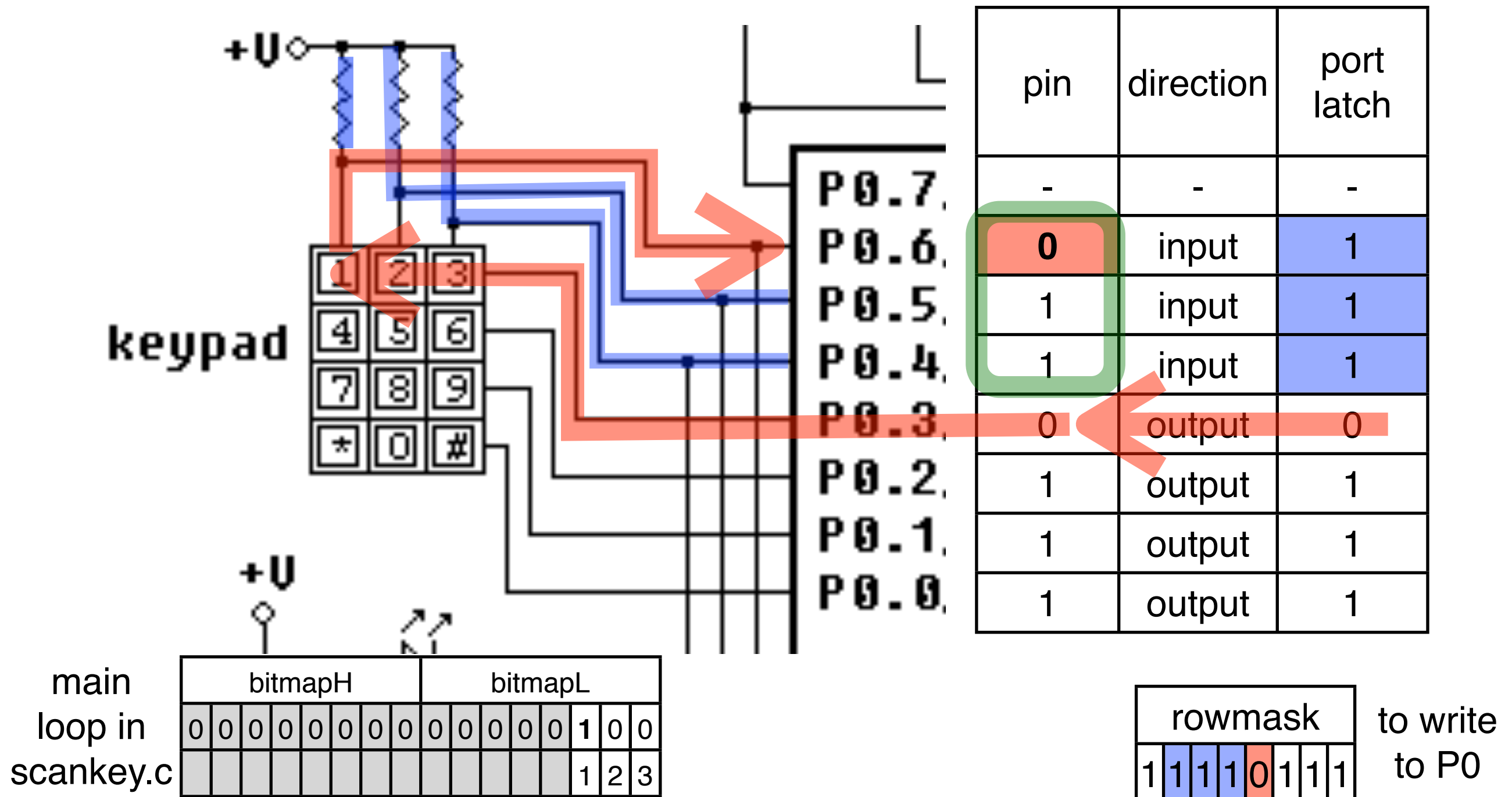


# Testing row 1 while key [1] pressed

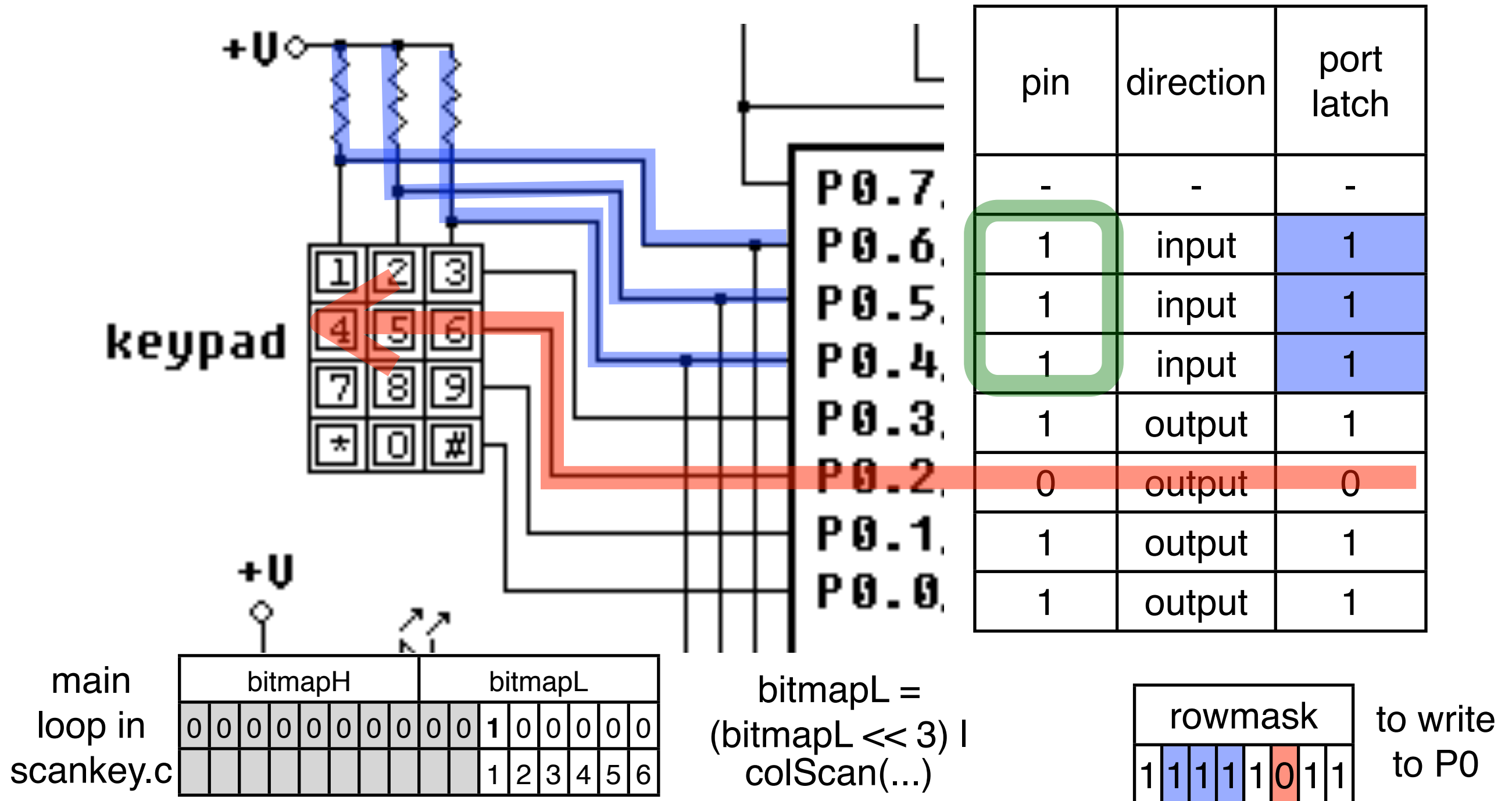

# Testing row 2 while key [1] pressed

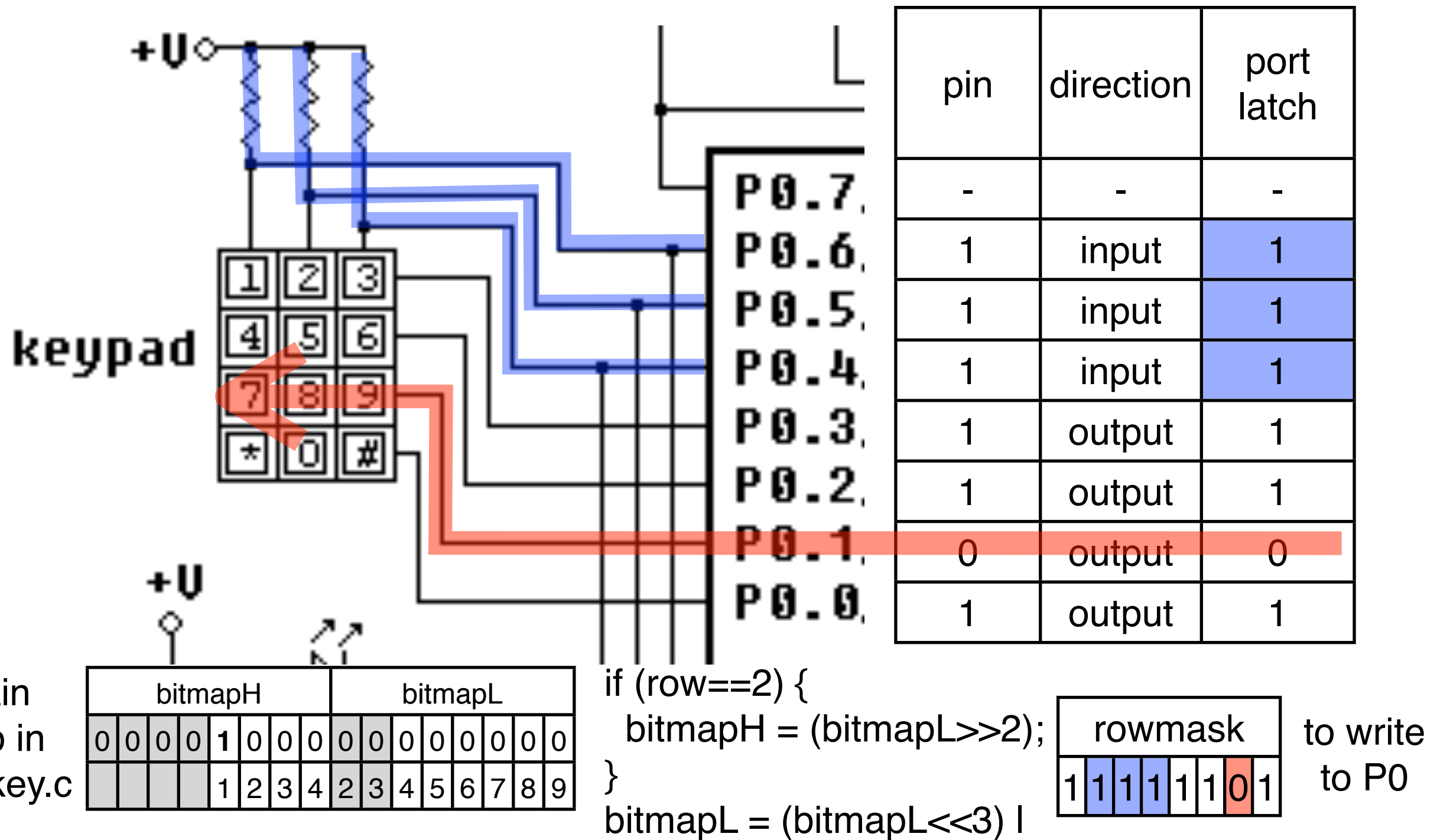

# Testing row 3 while key [1] pressed

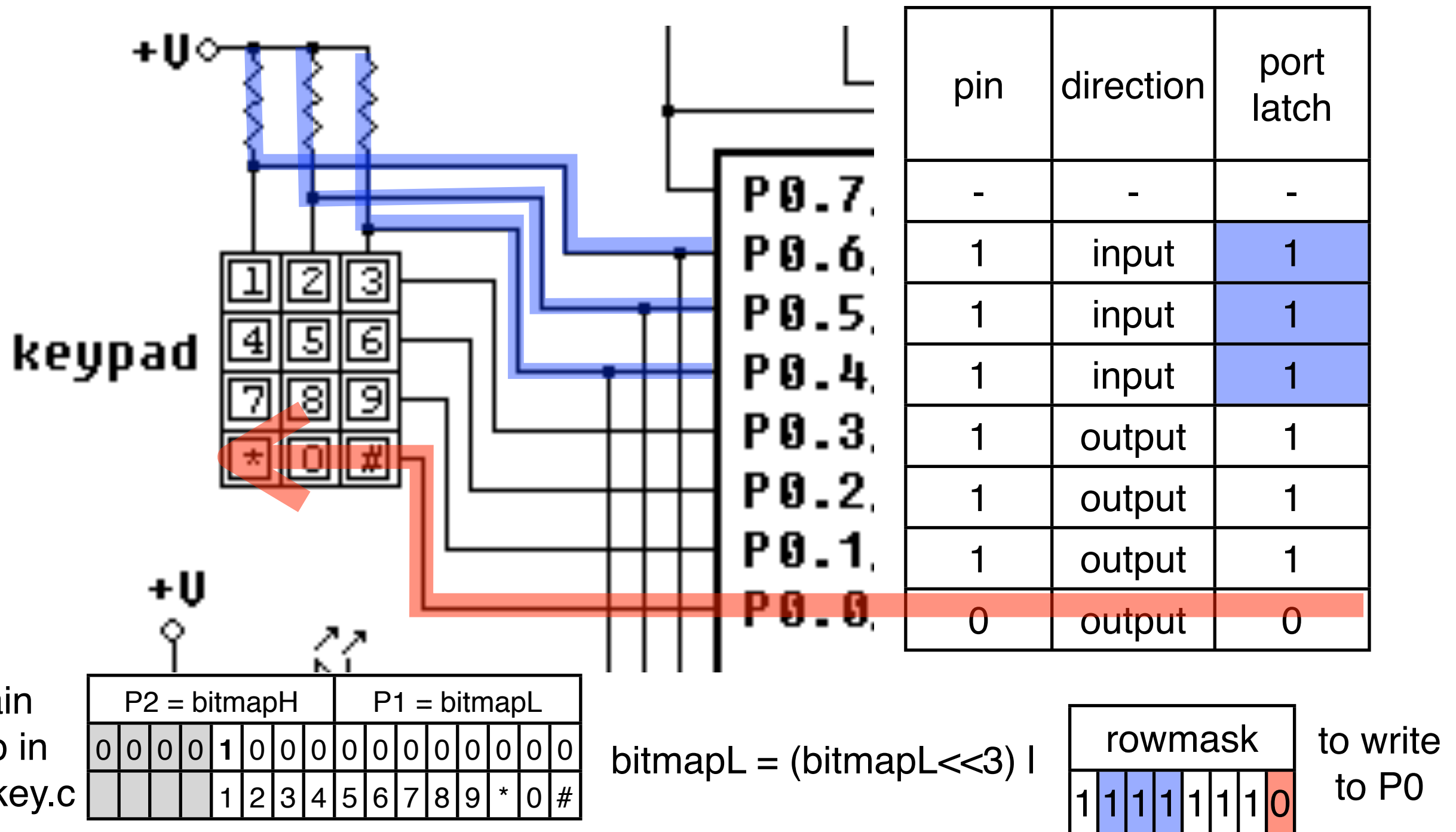


# Applying row/col multiplexing to LED

- Can control LEDs by row-col scanning
- Hardware solution
  - Use a hardware decoder or demultiplexer
- Software solution
  - Use row-column multiplexing


# EdSim Example: 7-segment LED

$A_{<1:0>} = P3_{<4:3>} = 11, CS = 1$

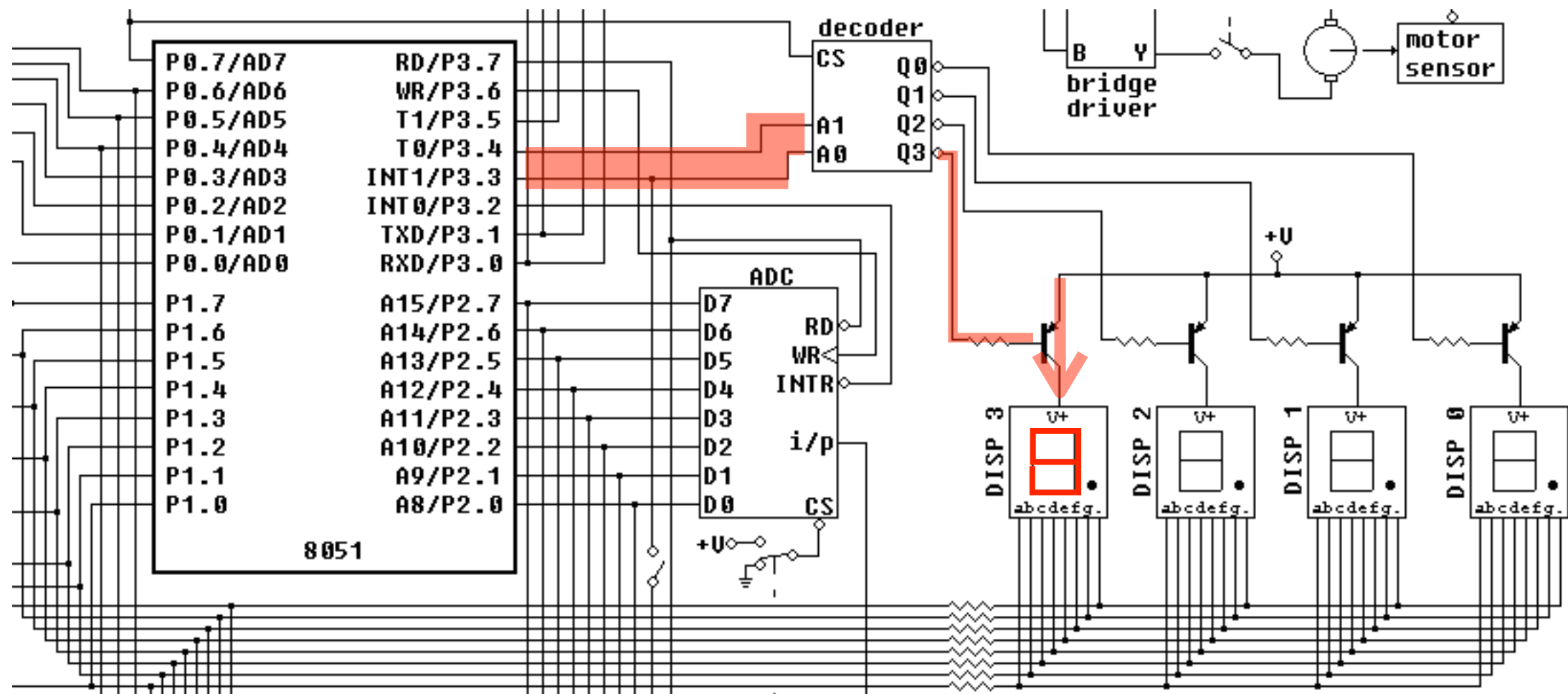

# EdSim Example: 7-segment LED

$A_{<1:0>} = 10$

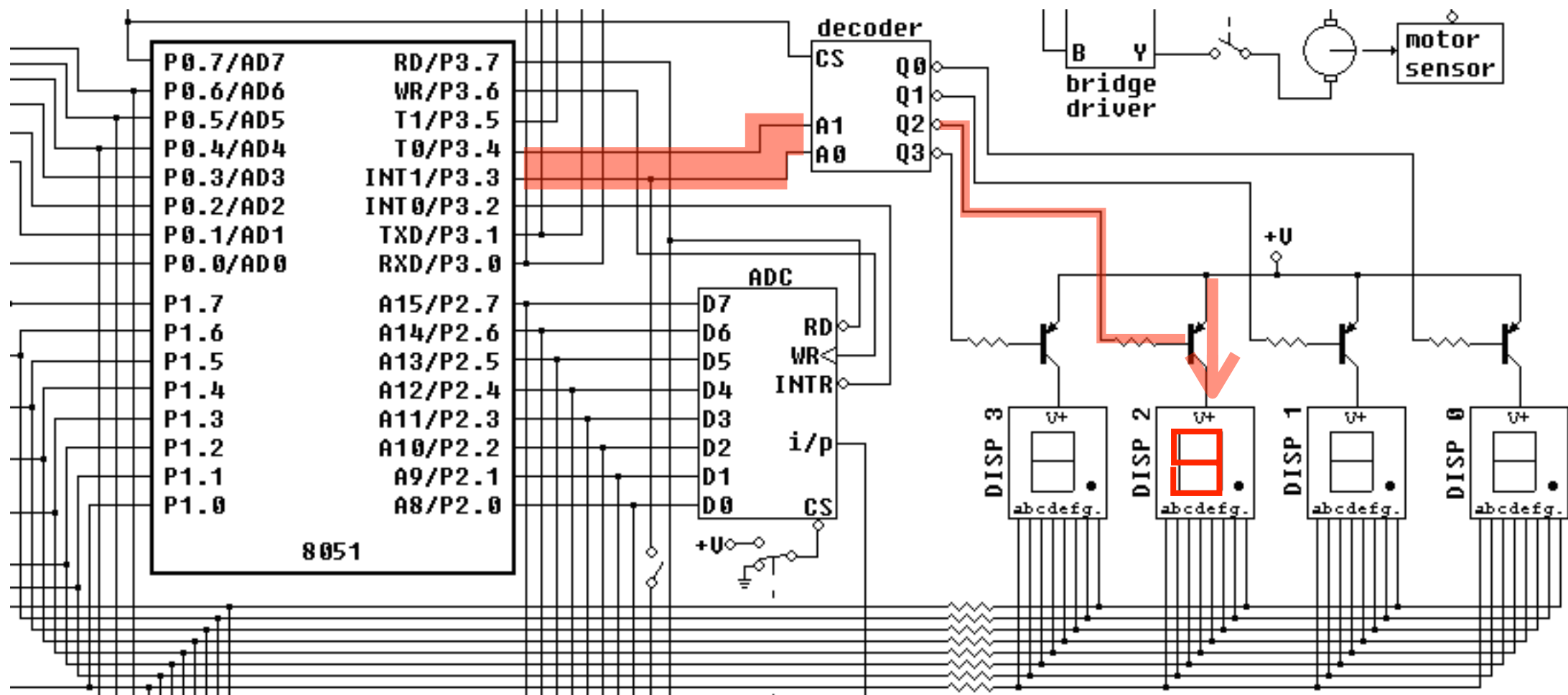




# Rapidly cycling through all digits

- Digits could appear to flicker
  - If fast enough, then eyes might not see flicker
- Frequency above flicker perception
  - 60 Hz (some can tell)
  - $\geq 200$  Hz -- most people can't tell.


# Software solution

- Analogous to row-column scanning
  - Difference: Row-column both output
- Connect LED from Row to Col
  - Row = 1, Col = 0 to turn LED on
  - Row = 0, Col = 1 to keep LED off


# Normally, LED off

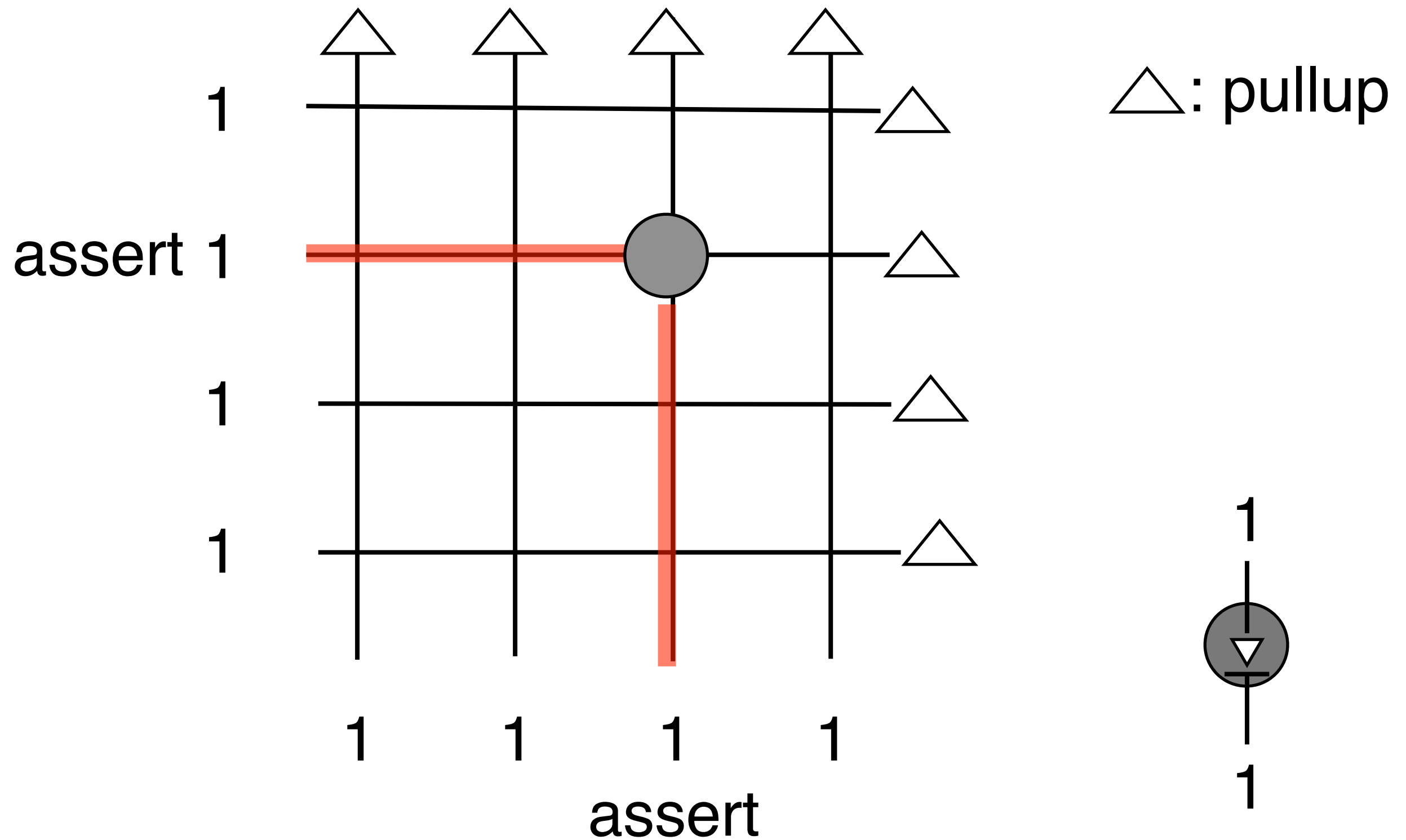


# LED Select

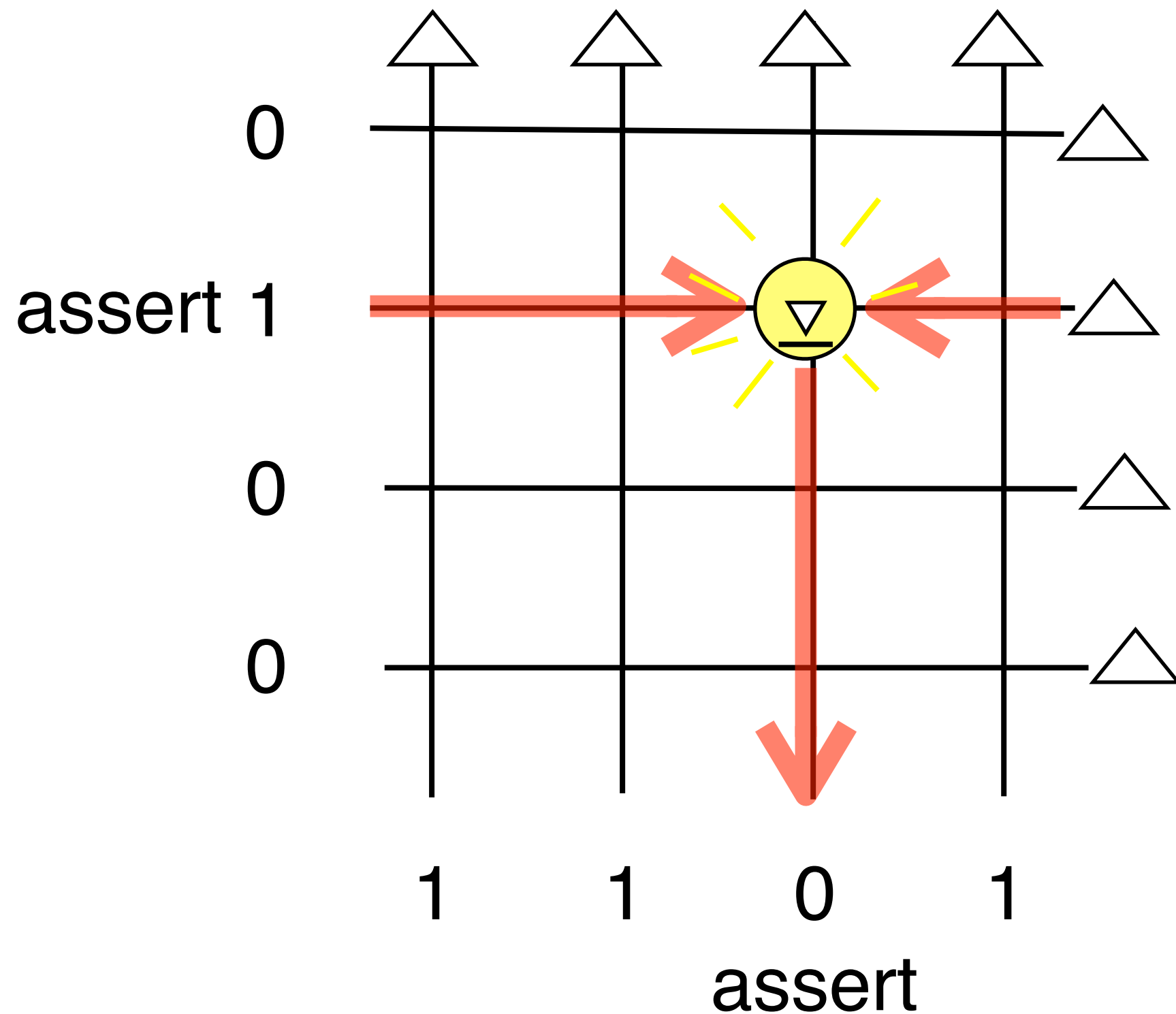

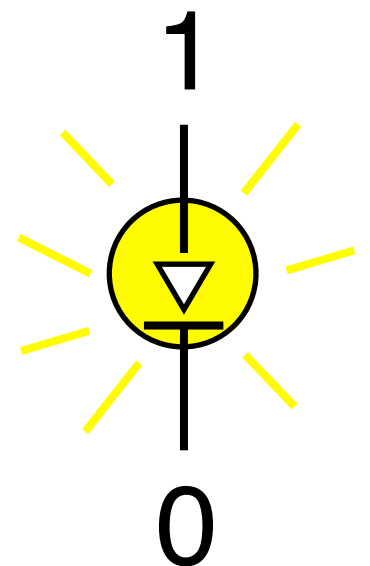
Loop the  
rows &  
columns  
to turn on  
one LED  
at a time




# LED unselected: case 1

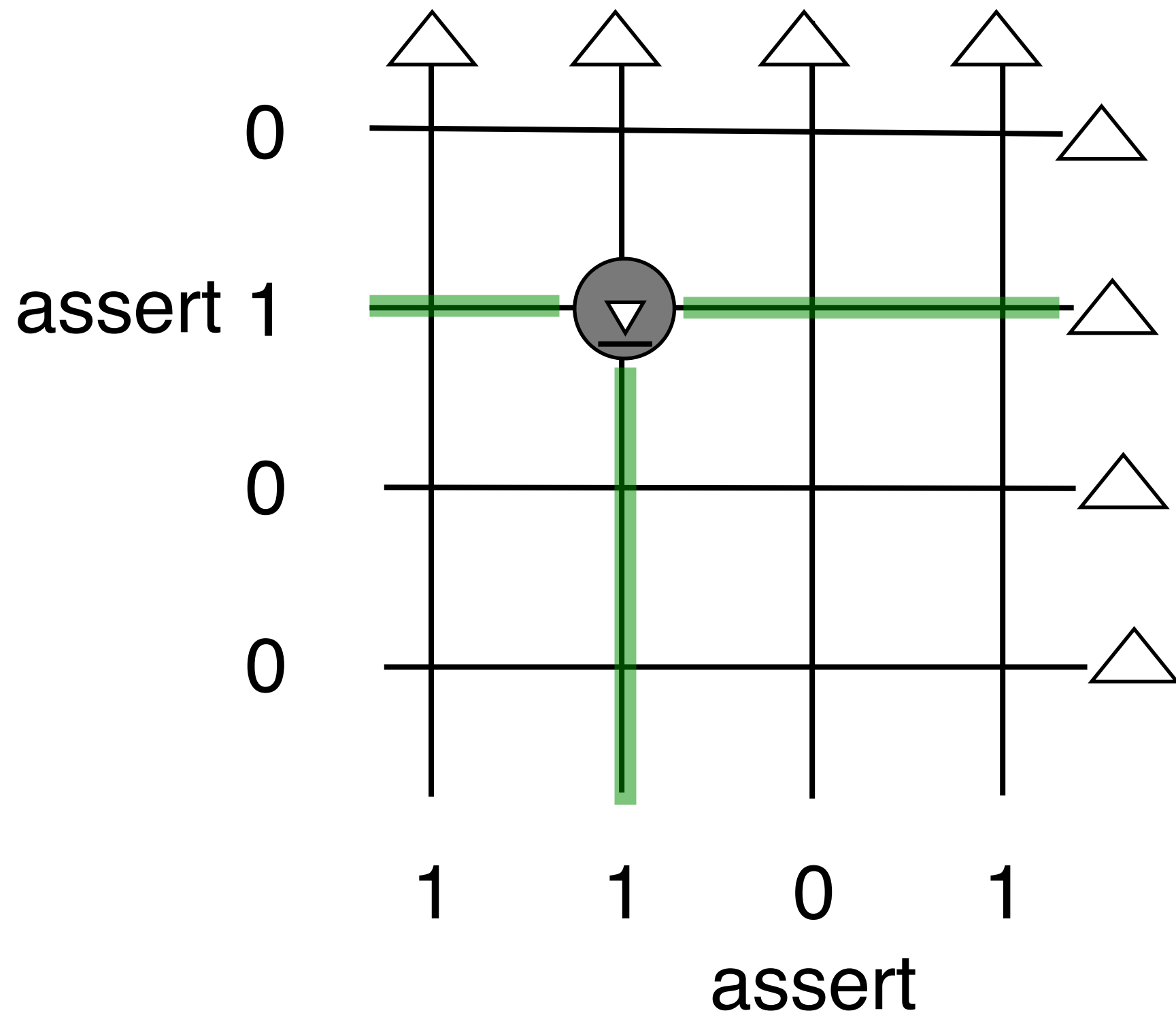

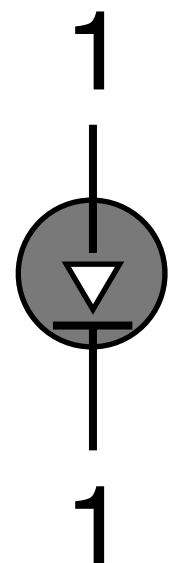
LED not lit  
because  
both sides are  
of the same  
high voltage!




# LED unselected: case 2

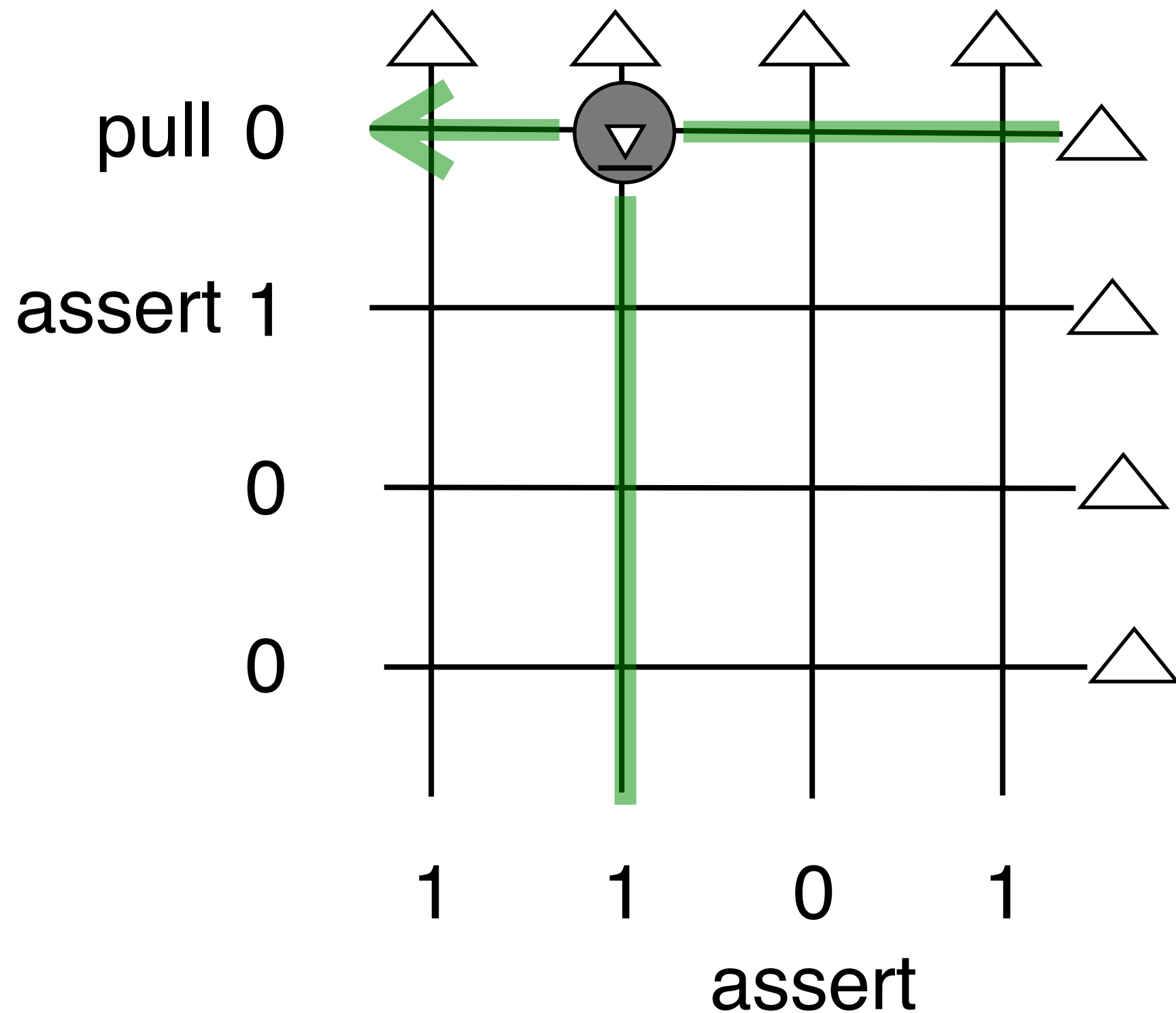

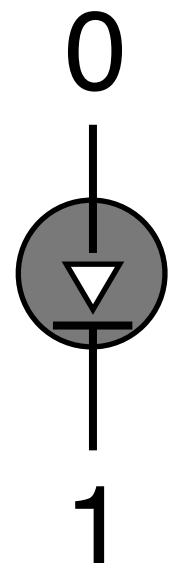
LED not lit  
because  
polarity is  
reversed!




# LED unselected: case 3

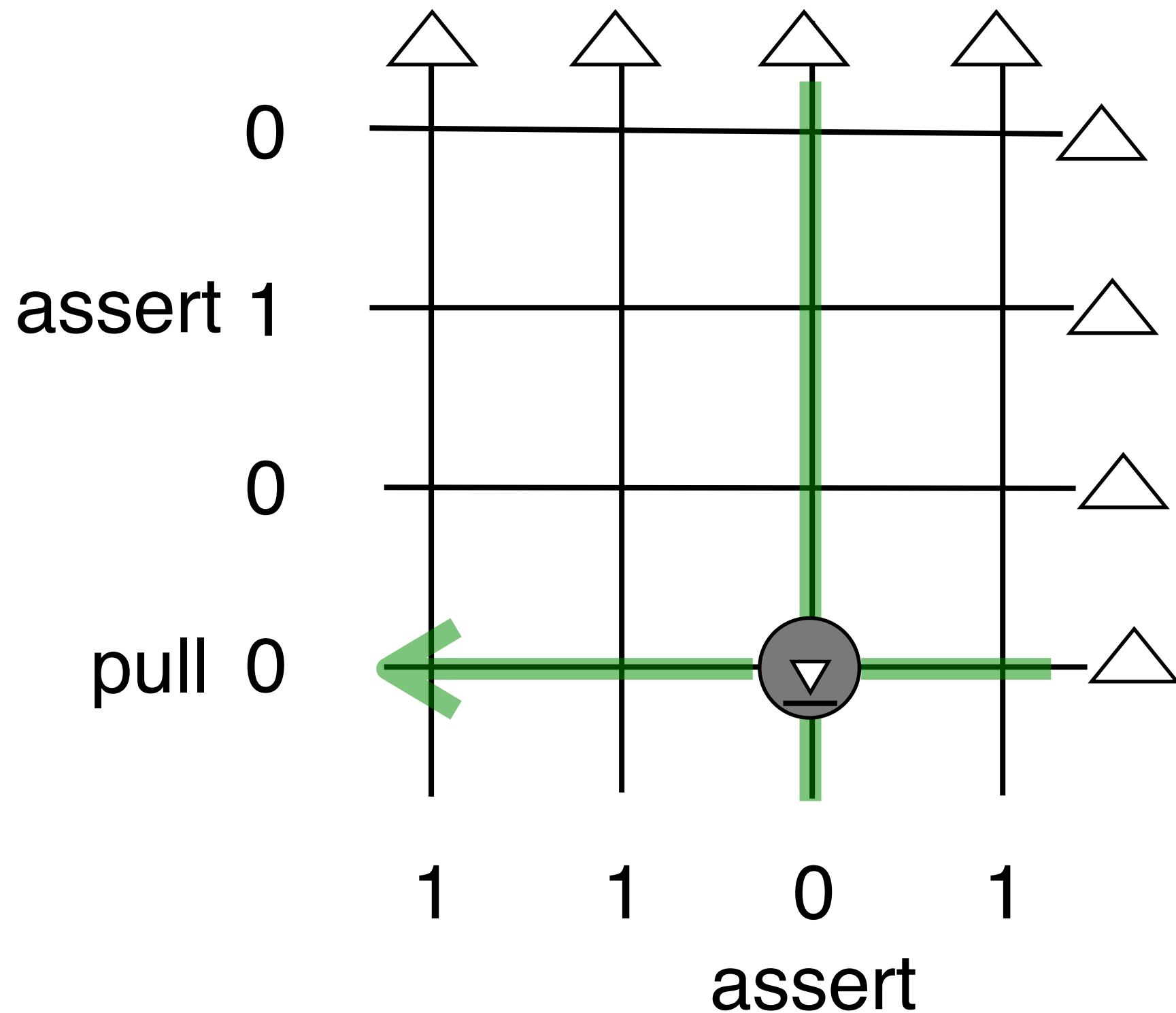

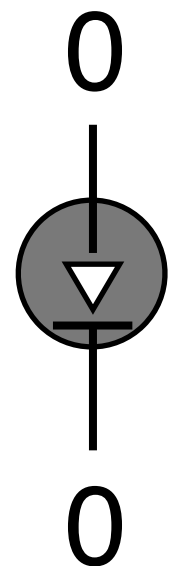LED not lit  
because  
both sides  
are of same  
low voltage



# Application of Row/Col: 3D Cube Light

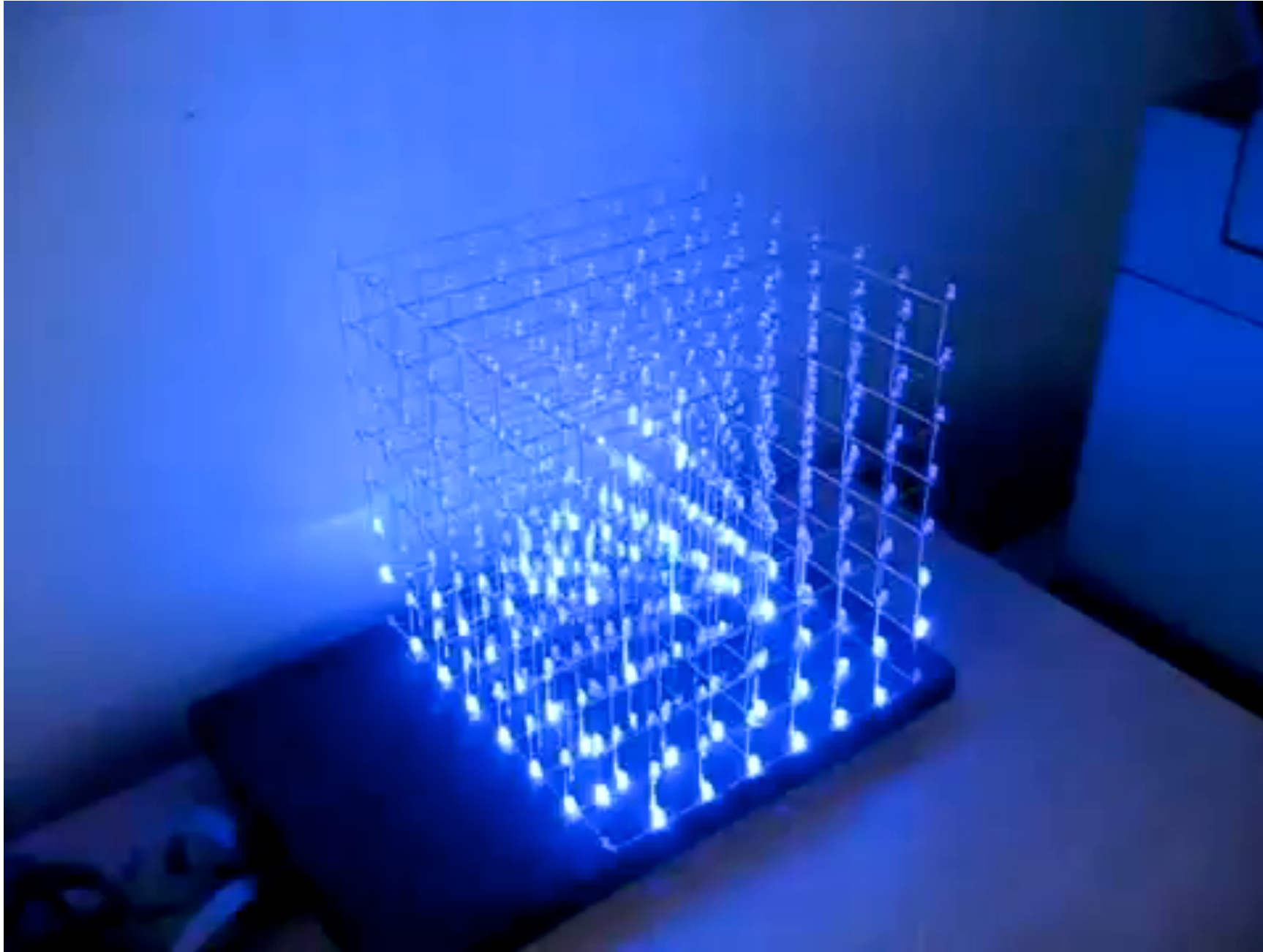




# Number of GPIO pins needed

- Usually,  $2 \times \text{square root of total pins}$ 
  - 8x8x8 cube:  $2 \times \text{sqrt}(512) = 2 \times 23 = 46$  pins
  - too many for original 8051 (32 GPIO)
- Alternative:
  - generalize schematic to 3D!!!


# Generalizing to 3D

x	y	z	state
0	0	0	off
0	0	1	off
0	1	0	off
0	1	1	off
1	0	0	off
1	0	1	off
1	1	0	on
1	1	1	off


△: pullup

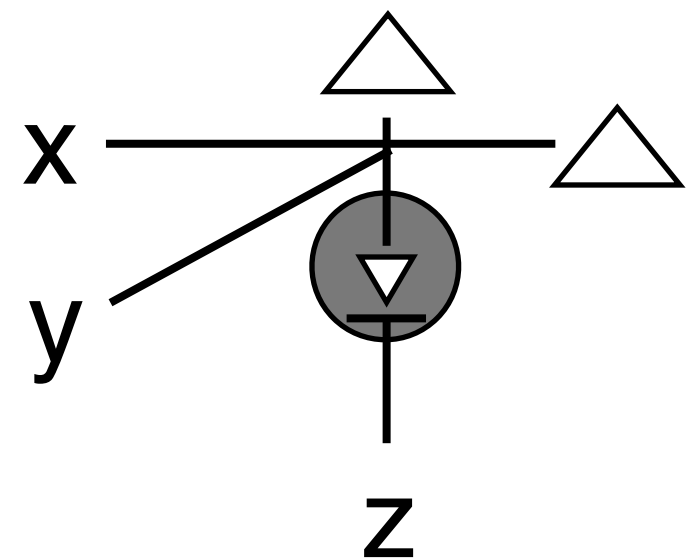


# Normally, LED off

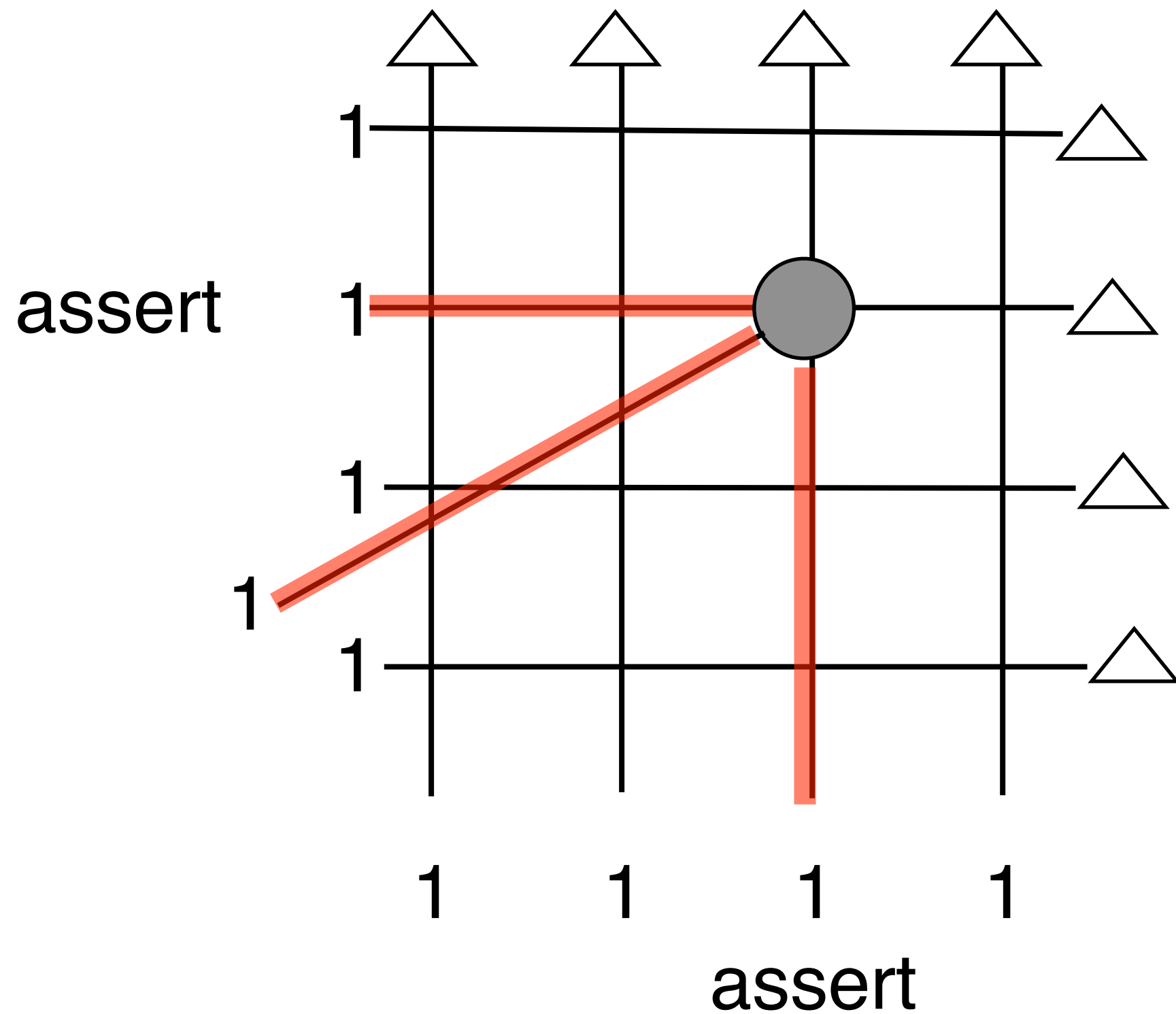


△: pullup

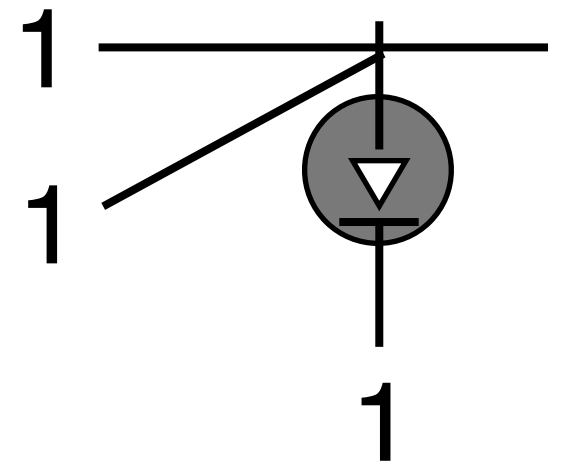


# LED Select

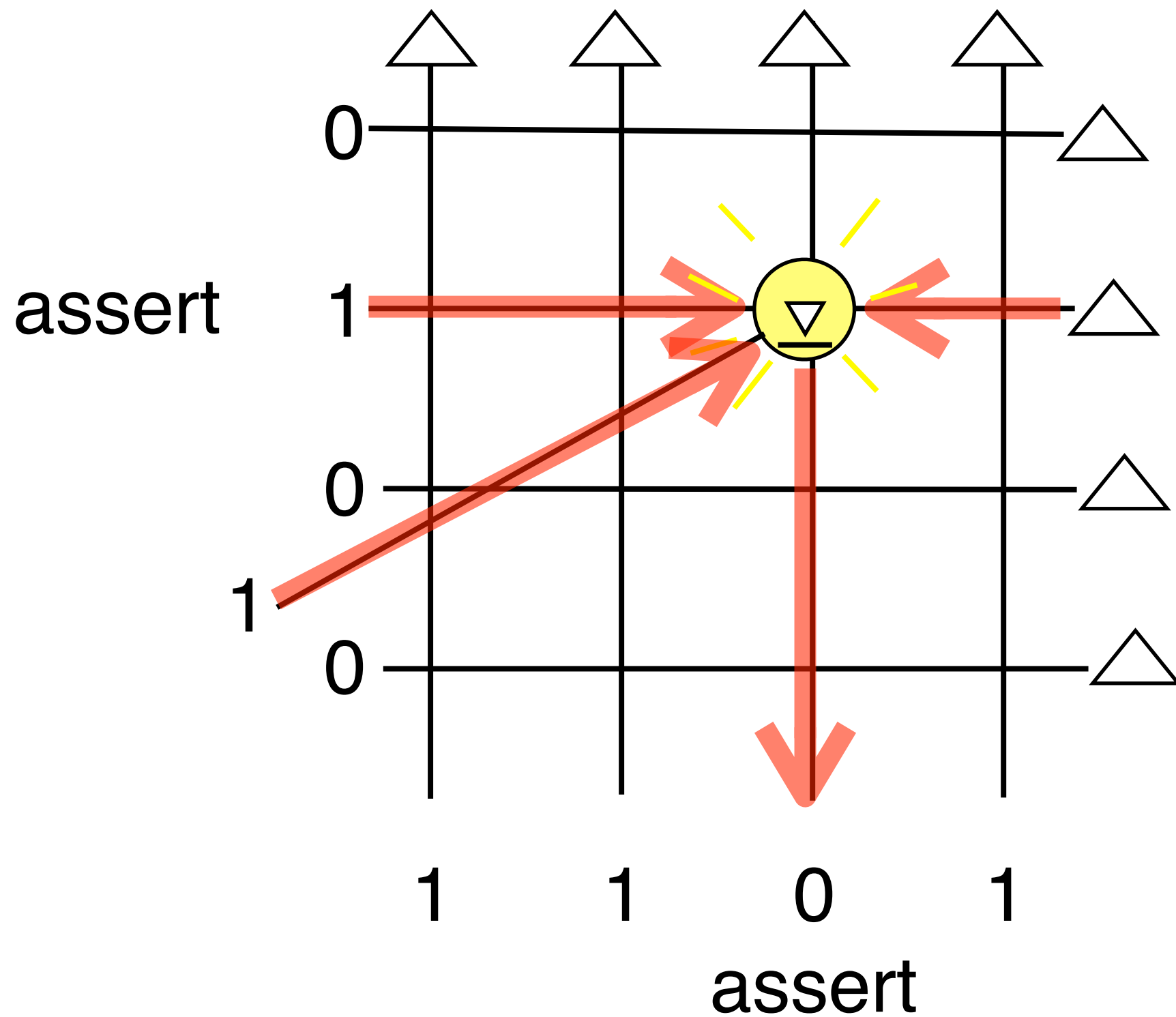

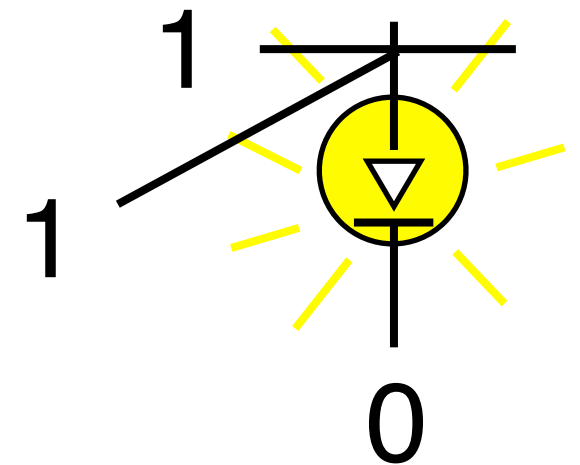
Loop the  
rows &  
columns  
to turn on  
one LED  
at a time




# LED unselected: case 1

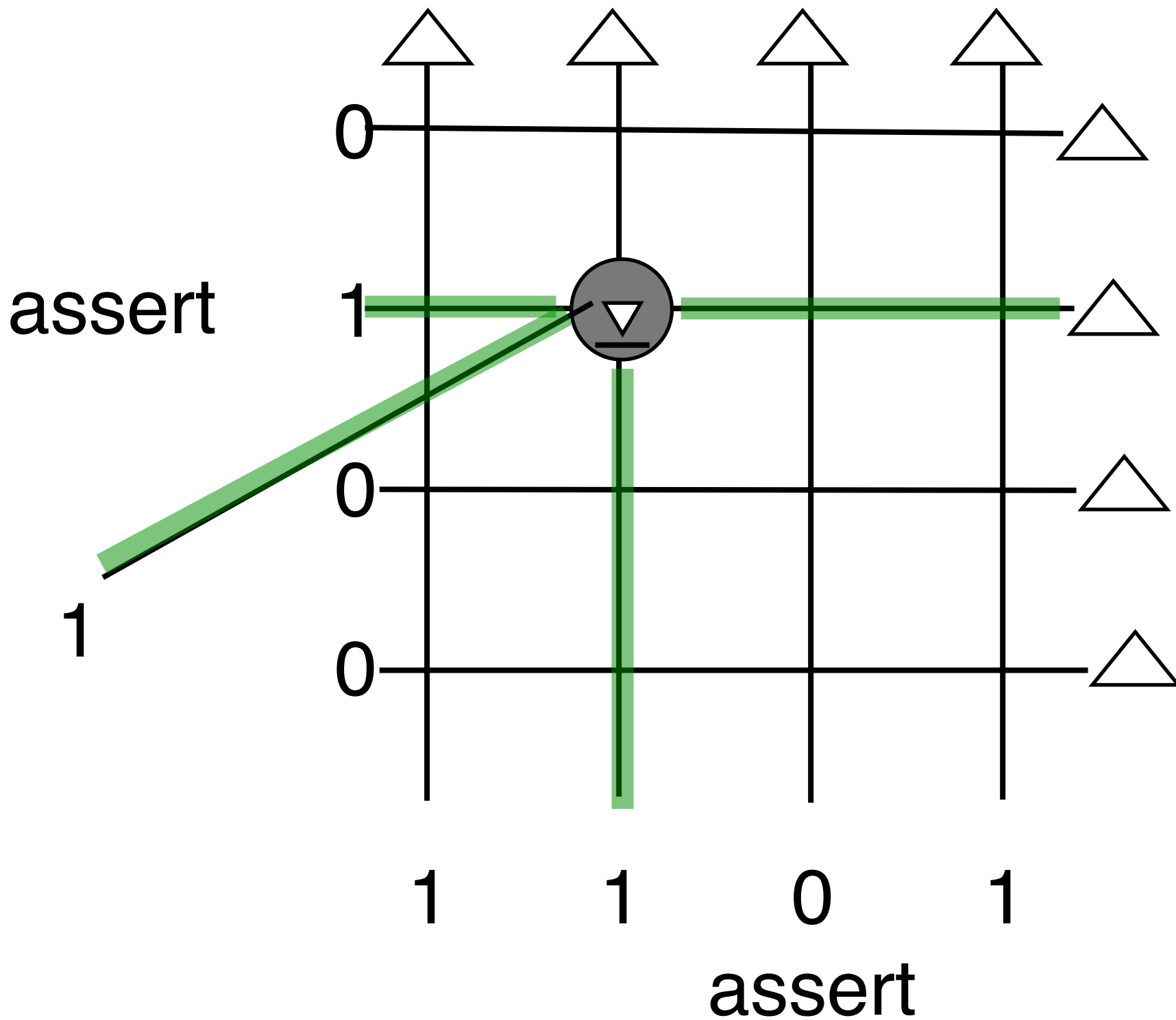

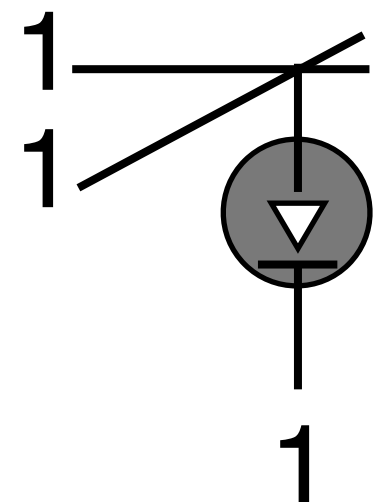
LED not lit  
because  
both sides are  
of the same  
high voltage!




# LED unselected: case 2

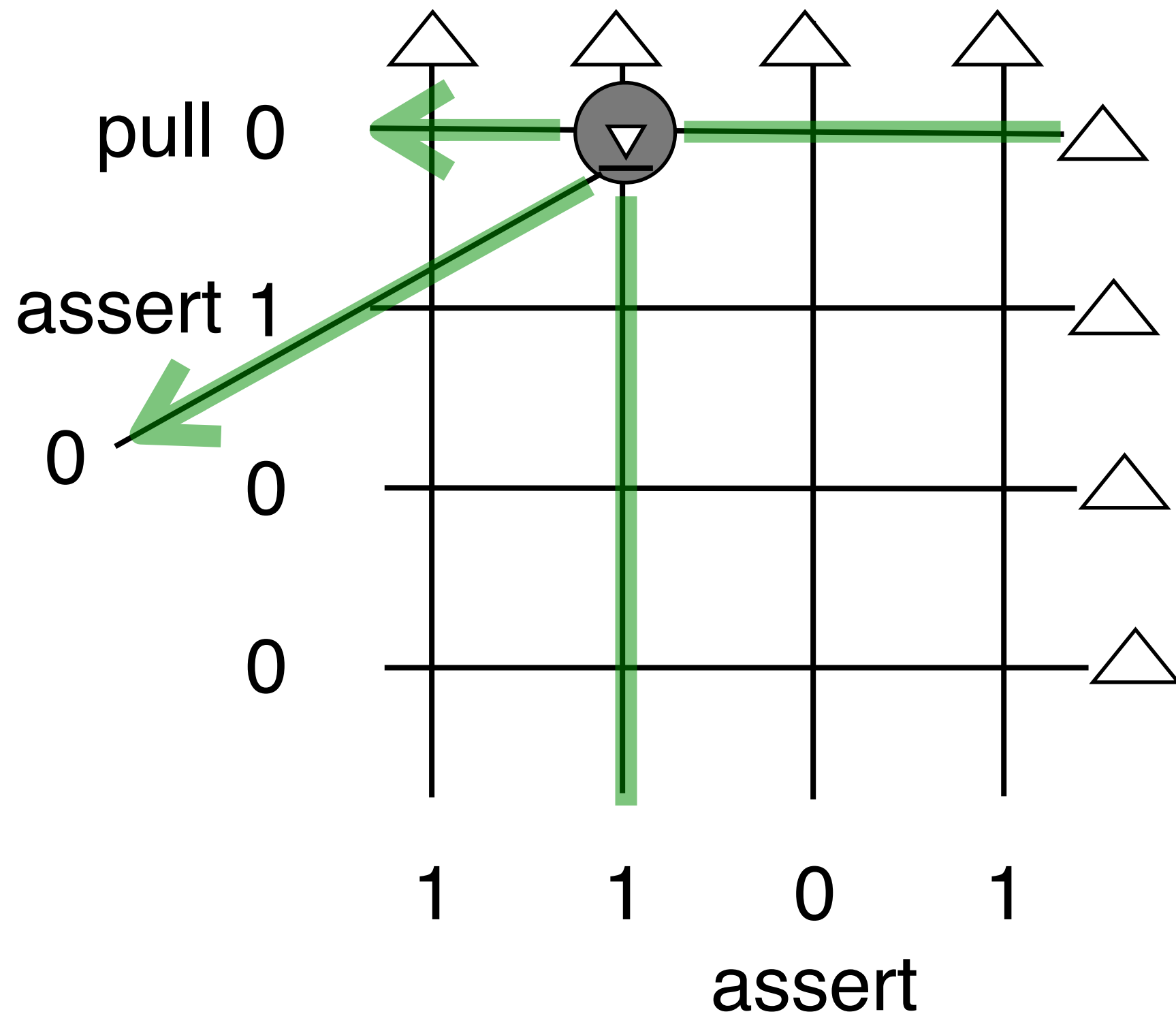

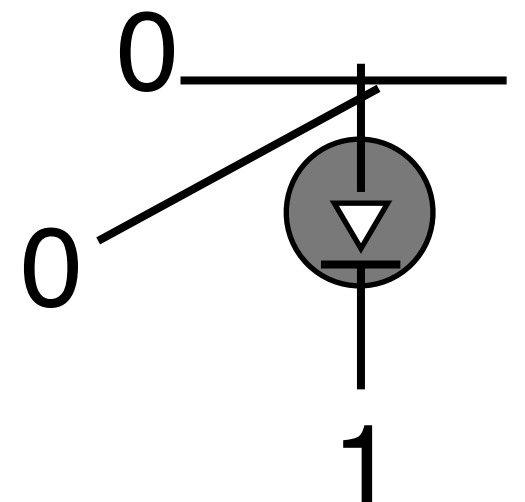LED not lit  
because  
polarity is  
reversed!



# LED unselected: case 3

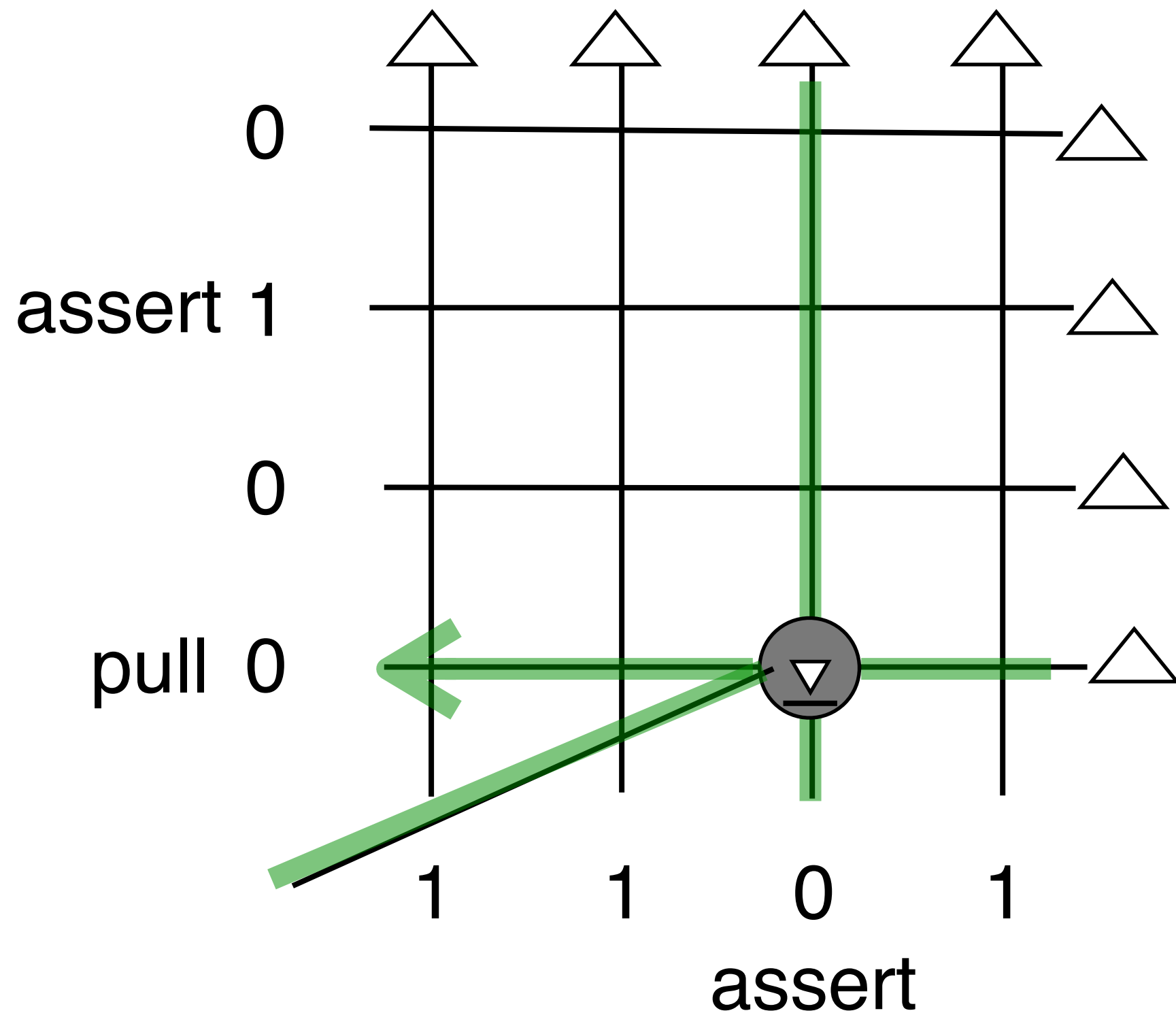

LED not lit  
because  
both sides  
are of same  
low voltage

